

VLSI Digital Design

MODULE V

TEST TECHNIQUES

- 5.1 Introduction.
- 5.2 Manufacturing test principles.
- 5.3 Design for test.
- 5.4 Self-test.
- 5.5 System-level test.


5.1 Introduction

5.1.1. Test motivation

“Rule of 10”

Detection level	IC fault cost
Wafer	0,01\$ ~ 0,1\$
Package	0,1\$ ~ 1\$
PCB	1\$ ~ 10\$
System	10\$ ~ 100\$
Field	100\$ ~ 1000\$

*Detect faults
as soon as possible!*

 


5.1.2. Functional test

- Behavior verification (Function-level specifications verification)

Example: Microprocessor instruction execution

5.1.3. Manufacturing test

IC manufacture → Inherent defaults

 


- IC gates and device verification

5.1 Introduction

Definitions:

Defect: Manufacturing error that produces out-of-range deviations in some device operation.


 
Fault: Incorrect IC operation due to defects.



A defect does not imply any fault necessarily

Verification in manufacturing test:

  - All gates correctly switch to both logic levels
- All registers correctly store both states



Other verifications:

- I/O level test (noise margin)
- Speed test
- Quiescent current test (I_{DDQ}), in complementary circuits.

Wafer- and package-level tests are possible.



5.1 Introduction

Test pattern: Applied input and expected output signals combination.

Test program: Set of applied vectors.


Exhaustive test: Verification of all possible system input and state combinations.

  Process yield: Percent of circuits that correctly perform the test program.



Cost example of exhaustive test.

Finite state machine:

 


It requires $2^{(n+m)}$ test patterns.

Not possible for most real IC's.

5.2 Manufacturing test principles

5.2.1. Fault models

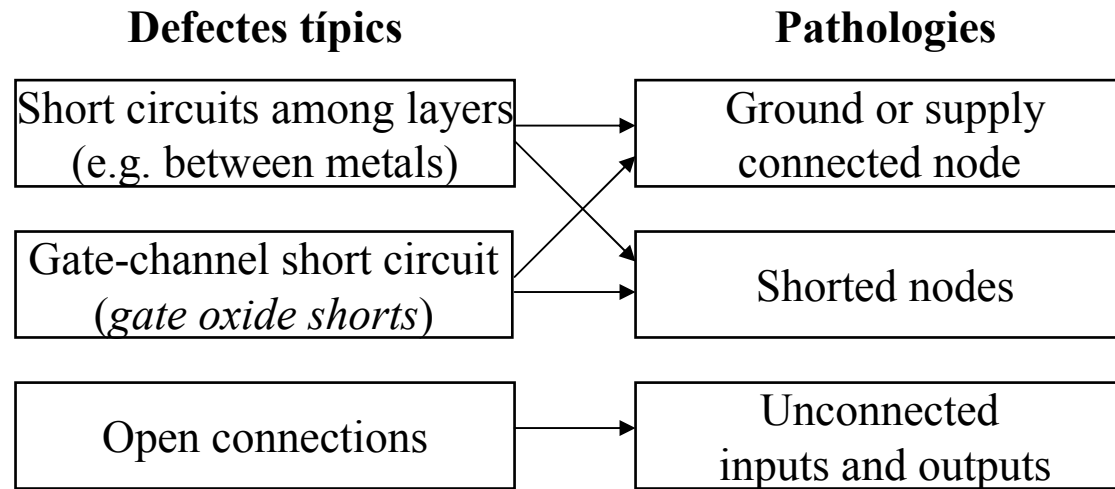

a) *Stuck-at* faults.

Historically, the most popular model.

- *Stuck-at-0*: Input value tied to '0', independently of the logic level applied from the circuit that controls its input.
- *Stuck-at-1*: Input tied to '1', independently of the logic level applied from the circuit that controls its input.


Physical causes:

- Metal shorts (with V_{SS} or V_{DD})
- Gate-channel shorts (NMOS gate with V_{SS} or PMOS gate with V_{DD}).

5.2 Manufacturing test principles

b) Bridge or open circuit faults.


More general than stuck-at.

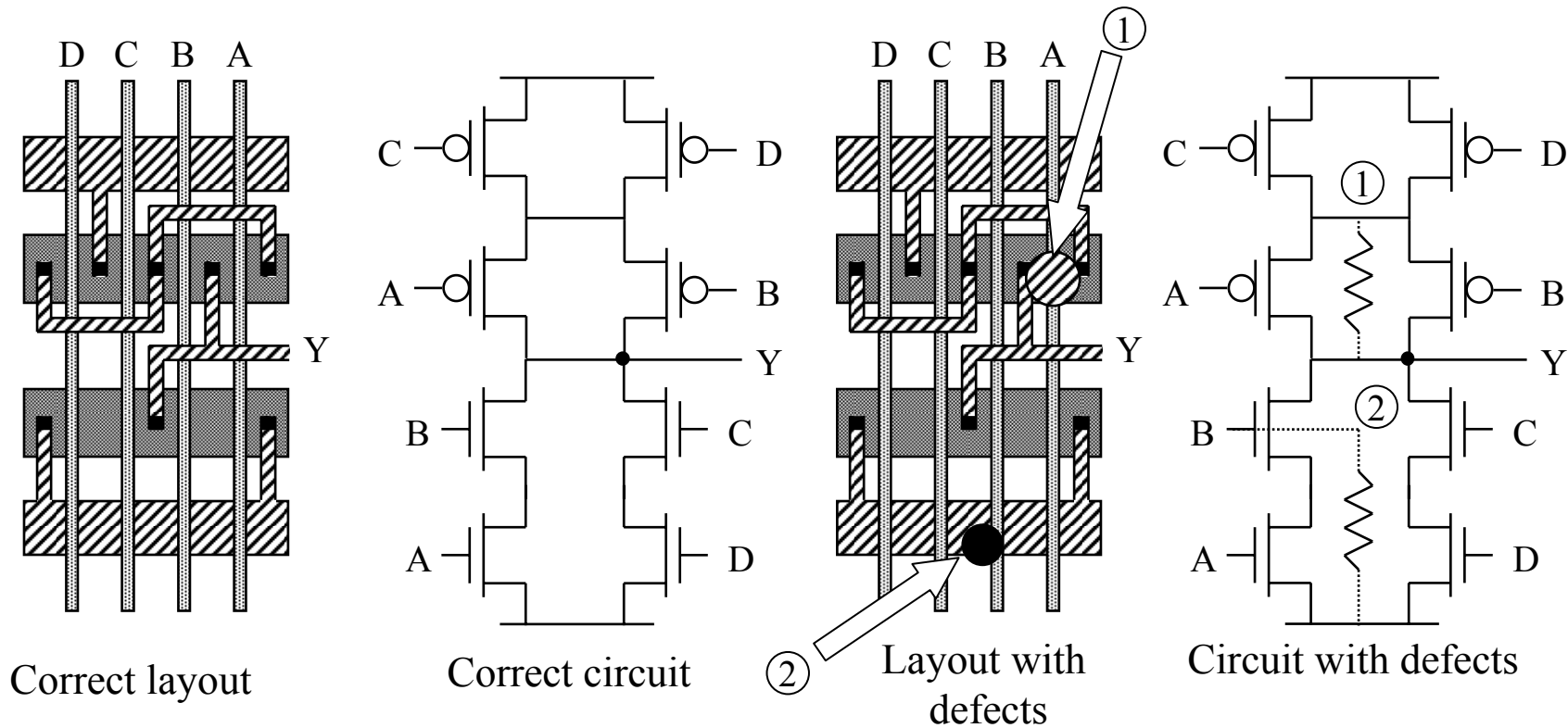

5.2 Manufacturing test principles

To cope with short or open faults transistor level models are required (or, at least, switch-level).



Example: Sequential fault.

 

$$Y = \overline{(A + B)} + A \cdot \overline{B} \cdot Y^- \rightarrow \text{depends on previous state}$$

```

  correct: process (A, B)
begin
  Y <= A nor B;
end process;
stuck_open: process (A, B)
begin
  if A='0' and B = '0' then Yso <= '1';
  elsif B = '1' then Yso <= '0';
  end if;
end process;
  
```



5.2 Manufacturing test principles

5.2.2. Fault coverage

Fault coverage: Fault percent that a test program can detect.

Fault coverage calculation:

1 Simulate

- The correct circuit
A single-fault circuit (e.g., stuck-at-0 at a single node).
- Fault is detect if some difference appears in an output node during the test.

2 Repeat the process for all possible circuit fault.

High CPU time → *stuck-at* fault model.
Problem: The *stuck-at* model does not guarantee every fault detection

5.2.3. Controlability and Observability

Controlability of a circuit node: Degree of simplicity/difficulty to fix its logic value to 0 or 1 applying logic values to inputs

Observability of a node: Degree of simplicity/difficulty to observe its logic value (propagating it to an output node).

There exist design techniques that make nodes easily controlables and observables.

A possible definition for **SCOAP** controlability and observability, is shown in the following.

5.2 Manufacturing test principles

5.2.4. SCOAP algorithm. Method of controllability and observability assignment.

- Static (combinational). Definitions:
 - $CC0(n)$. Node n combinational controllability to 0.
 - $CC1(n)$. Node n combinational controllability to 1.
 - $CO(n)$. Node n combinational observability.
- Dynamic (sequential). Definitions:
 - $SC0(n)$. Node n sequential controllability to 0.
 - $SC1(n)$. Node n sequential controllability to 1.
 - $SO(n)$. Node n sequential observability.

Controllability and observability calculation example: AND gate

$$CC1(z) \equiv CC1(a) + CC1(b) + 1$$


$$CC0(z) \equiv \min[CC0(a), CC0(b)] + 1$$

$$CO(a) \equiv CO(z) + CC1(b) + 1$$

$$SC1(z) \equiv SC1(a) + SC1(b)$$

$$SC0(z) \equiv \min[SC0(a), SC0(b)]$$

$$SO(a) \equiv SO(z) + SC1(B)$$

 

1 is added to static definitions because the AND gate represents a combinational logic level.


5.2 Manufacturing test principles

Circuit calculation process:


1. Controlabilities are calculated starting from the primary inputs. ($CC0 \equiv 1$, $CC1 \equiv 1$).
2. Observabilities are calculated starting from the primary outputs $CO \equiv 0$.

Example.


Combinational controlability to 1 (CC1):

 

Combinational controlability to 0 (CC0):

 

Combinational observability (CO):

 

5.2 Manufacturing test principles


Observations:

- For multiple fanout output, the smaller observability measure is taken.
- High controllability (observability) values indicate difficulty to control (observe).
- Good testability is related with good controllability and observability, but not directly.
Exceptions: Redundant circuits.

Exercise


- Calculate CC_0 , CC_1 i CO for an XOR gate and for 2- 3-input NAND gates.
- Calculate CC_0 , CC_1 i CO of a full adder.
- Obtain for an n-bit carry propagate adder the maximum value of CC_0 , CC_1 i CO as a function of n.

Justify the answers.

 

 5.2 Manufacturing test principles

SCOAP calculation example for a sequential circuit



Node	CC0	CC1	CO	SC0	SC1	SO
CK	1	1	29	0	0	10
X1	1	1	20	0	0	7
X2	13	26	8	4	8	3
Y	15	2	6	4	0	3
Q1	17	4	4	5	1	2
Q2	19	6	2	6	2	1
Q3	21	8	0	7	3	0

5.2 Manufacturing test principles

5.2.5. Automated Test Pattern Generation (ATPG)

D algorithm

Consists in propagating logic level differences between the correct and faulty circuit

5 logic values : 0, 1, D, /D, X

- D: 1 at correct system, 0 at faulty system
- /D: 0 at correct system, 1 at faulty system
- X: Undefined

Examples:

AND function


A\B	0	1	X	D	/D
0	0	0	0	0	0
1	0	1	X	D	/D
X	0	X	X	X	X
D	0	D	X	D	0
/D	0	/D	X	0	/D

OR function

A\B	0	1	X	D	/D
0	0	1	X	D	/D
1	1	1	1	1	1
X	X	1	X	X	X
D	D	1	X	D	1
/D	/D	1	X	1	/D

5.2 Manufacturing test principles

 Example: S-A-0 (Stuck-at-0) detection at node h



h has to be set to 1 (to generate D):

$[a,b,c,d] = [1,1,1,0], [1,1,0,1]$ o $[1,1,1,1]$

and propagate D to the y output:

$[e] = [1]$

The test pattern is thus

$[a,b,c,d,e] = [1,1,1,0,1],$
 $[1,1,0,1,1]$ or
 $[1,1,1,1,1].$

For all internal nodes S-A-0 and S-A-1:

Node	Test	Pattern(s)
f	S-A-0	$[1,1,X,1,1], [1,1,1,X,1]$
f	S-A-1	$[0,X,X,1,1], [0,X,1,X,1],$ $[X,0,X,1,1], [X,0,1,X,1]$
g	S-A-0	$[1,1,1,X,1], [1,1,X,1,1]$
g	S-A-1	$[1,1,0,0,1]$
h	S-A-0	$[1,1,1,X,1], [1,1,X,1,1]$
h	S-A-1	$[0,X,X,X,1], [X,0,X,X,1],$ $[X,X,0,0,1]$


The pattern set

$\{[1,1,0,0,1], [1,1,0,1,1], [0,0,1,0,1]\}$

permits detecting all possible stuck-at faults in nodes f , g and h .

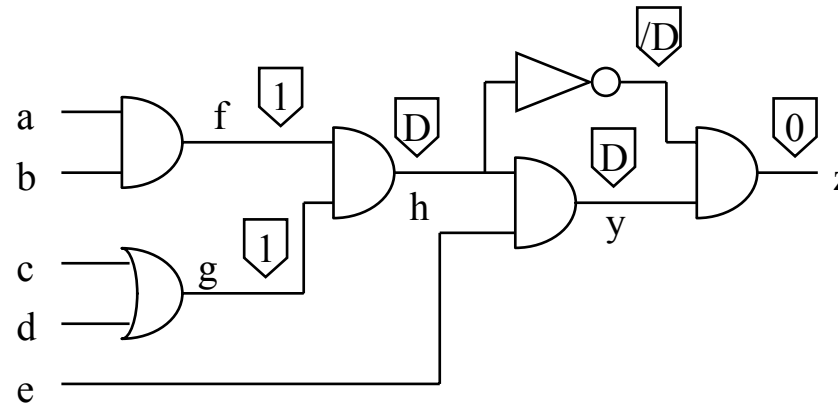5.2 Manufacturing test principles

Testability problem in redundant circuits :



Test pattern generation steps:

- Internal node **D** value propagation to a primary output (**sensitized path**). As a function of previously-calculated controllability figures, the gate path propagation is decided.
- **Primary input values determination** to uncover the fault and make it observable. This is done by **backtracing** from the faulty node and the sensitized path to the primary inputs using the controllability indexes of each node.

5.3. Design for testability

5.3.1. Design For Testability (DFT)

DFT techniques:

- Ad-hoc techniques
- *Scan-path* type
- Self test and *built-in* test

5.3.2. Ad-hoc test

Collection of ideas to improve controllability and observability. It comprises:

- Large sequential circuit partition
- Test point insertion
- Multiplexer insertion
- Reset state

Typical examples:


Large counters.

- Parallel load allows controlling easily the internal state.
- Intermediate point observation. Permits reducing the test length.

Bus-based systems.

- To allow applying inputs and reading outputs from all the elements connected to the bus.

Subsystem partition with multiplexers:

 

5.3. Design for testability

Reset need:

- Test
- System initialization to a known state

Ad-hoc techniques are fine for reduced complexity designs.


Complex designs demand **systematic approaches**.

5.3.3. Scan-based test

Consists in substituting the circuit flip-flops by dual input and input-clock **flip-flops**.

This permits building a *scan chain* independent of the system normal operation..

Basic block :

 

L1: *Master*. Double input port.

- D₁: Data input
- C₁: Data clock (phase 1)
- D'₁: Scan input
- C'₁: Scan clock (phase 1)



C₁ i C'₁ cannot be simultaneously active.

L2: *Slave*

- D₂: Data input
- C₂: Data/scan clock (phase 2)

5.3. Design for testability

Scan chain

 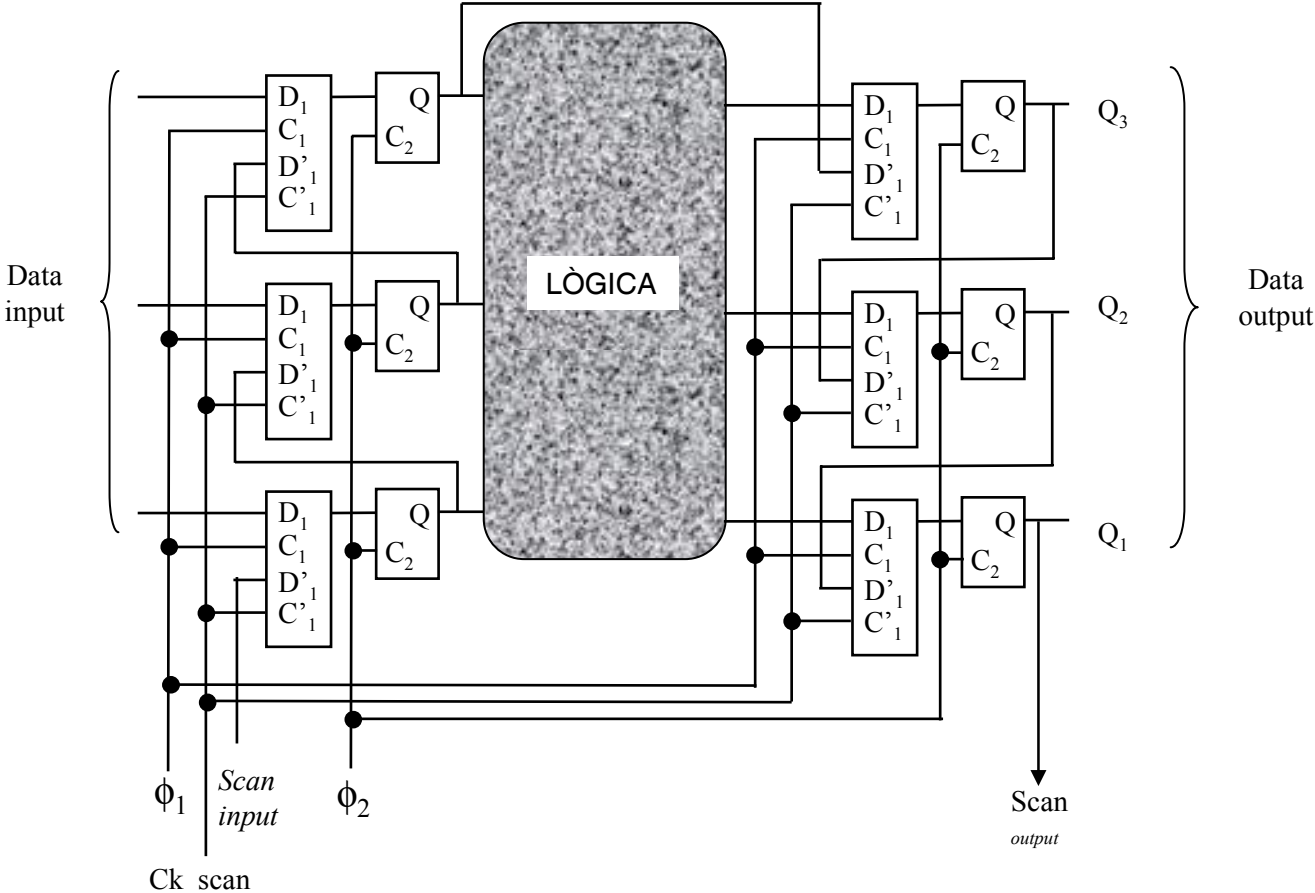

5.4. Self test


Test-specialized circuits are included into the IC for self verification. It requires:

- Test pattern generation
- Correct output verification (signature analysis)

5.4.1. Pseudo-random sequence generation

Pseudo-random sequence generator: LFSR (Linear Feedback Shift Register).

3 bit LFSR example:

 


- Low-cost test pattern generation method
- Also used for signature analysis.
- *For* n flip-flops, $2^n - 1$ vectors (states) are generated before the state repeats.

5.4. Self test


LFSR coefficient table:

n	s	Binary
1	0,1	11
2	0,1,2	111
3	0,1,3	1101
4	0,1,4	11001
5	0,2,5	101001
6	0,1,6	1100001
7	0,1,7	11000001
8	0,1,5,6,8	110001101
9	0,4,9	1000100001
10	0,3,10	10010000001
16	0,2,3,5,16	10110100000000001
32	0,1,27,28,32	110000000000000000-- 00000000000110001

Circuit structure:

 

Example: 8-bit LFSR

 

5.4.2. Signature analysis


Cyclic sum of circuit under test (CUT) outputs.

For each test pattern (e.g., generated with an LFSR), outputs are XOR'ed with previous results.

Syndrome: Test sequence resulting number. Can be stored in ROM.

A faulty circuit will generate, with very high probability, a syndrome value different than the correct circuit.


Example:

 

 5.4.3. Built-In Logic Block Observation (BILBO)

It combines:


- Pseudorandom sequence generation
- Signature analysis
- Shift register



MODE	C_0	C_1	
A	0	0	Scan
B	0	1	Reset
C	1	0	LFSR or signature analysis
D	1	1	Parallel register

5.4. Self test

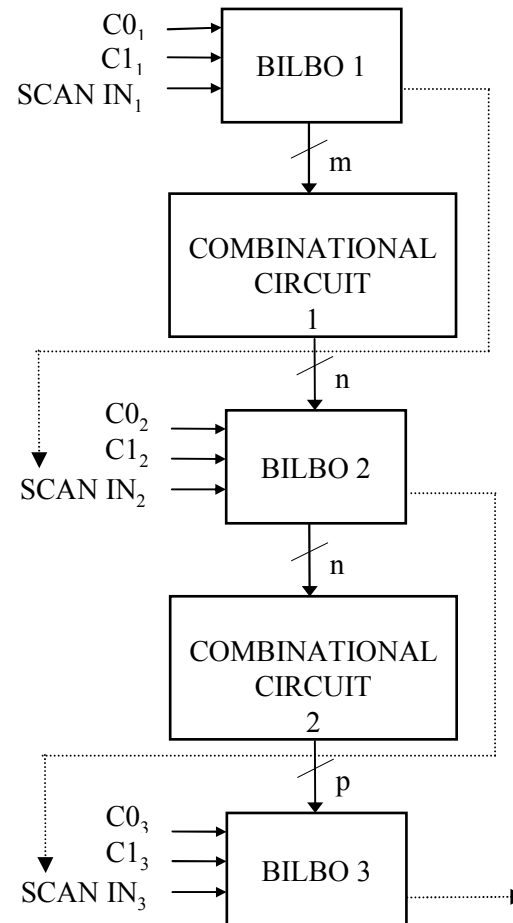Example: Registers replaced by BILBO in a pipeline.



5.5. System-level test


5.5.1. Boundary Scan

Unified methodology based on *scan* to verify ICs at PCB level.

Standard IEEE 1149 (JTAG): It defines a Boundary Scan architecture.

I/Os can be interconnected to form shift registers. This allows:

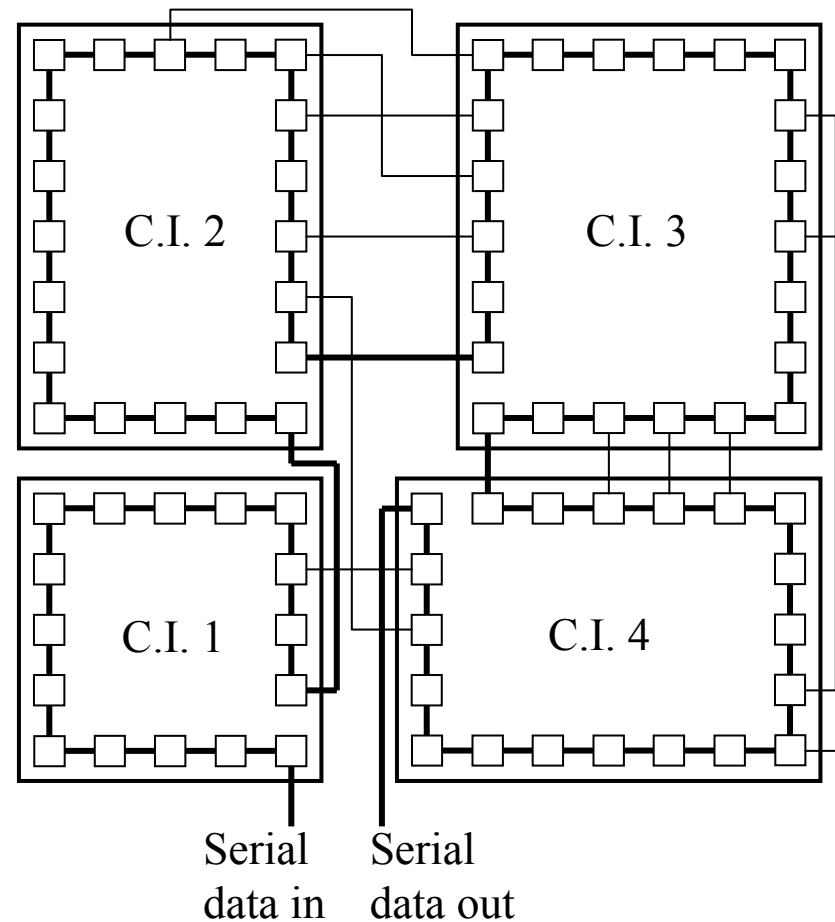- Connectivity tests among components
- I/Os capturing and loading
- Self-test data distribution and result extraction.




5.5. System-level test

5.5.2. Boundary Scan Architecture

Consists of:

- Boundary register
- Data register
- Test Access Port (TAP)
 - Instruction register
 - Bypass register
 - TAP controller
- I/O pins: TDI, TDO, TMS, TCK
 - Optionally TRST

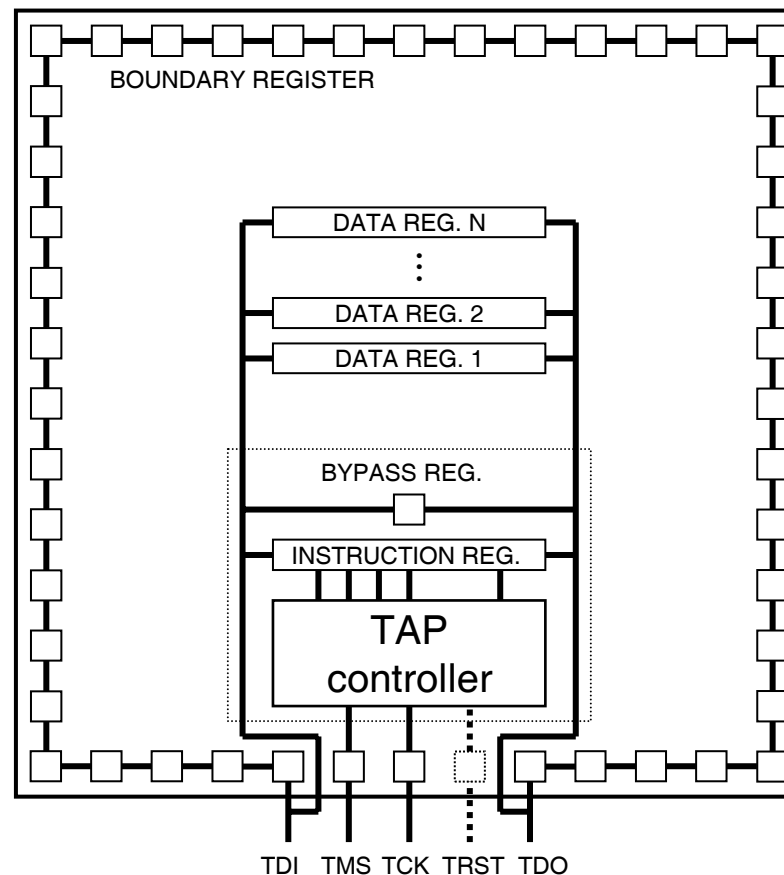Registers are built with BSCs
(Boundary Scan Cells)






5.5. System-level test

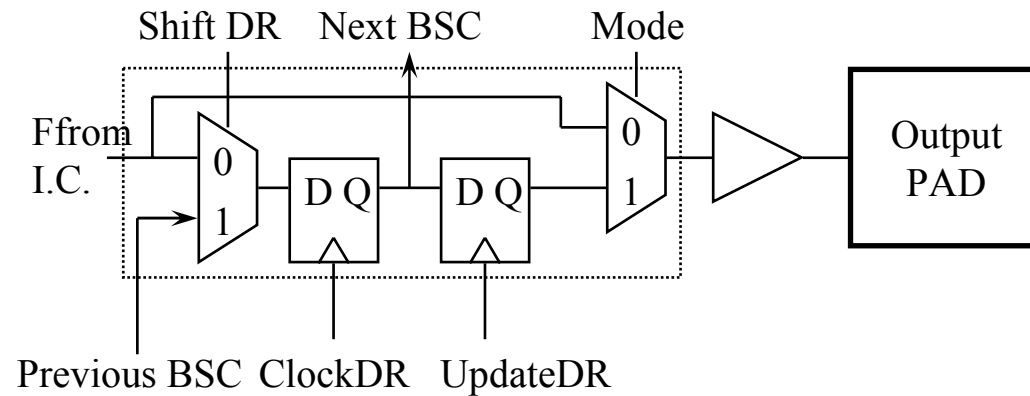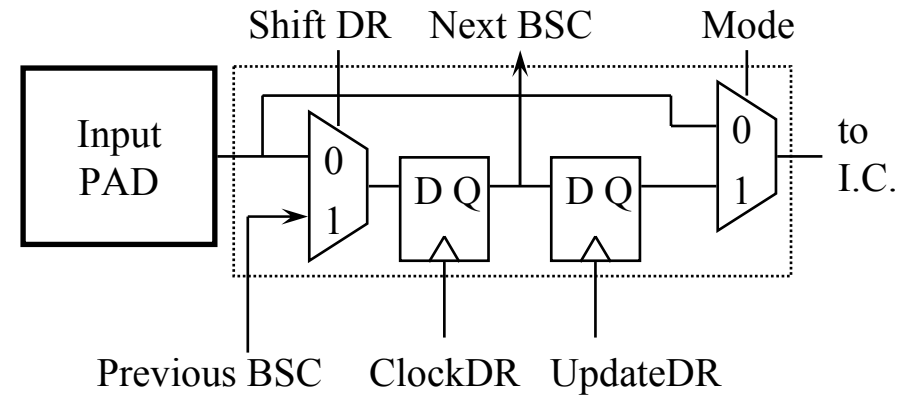 5.5.3. Boundary Register


Surrounds the IC through all I/O pads..

Boundary Scan Cells (BSC) are included in pads.




 5.5. System-level test

For a tristate output pad, two BSCs are required



 In a bidirectional pad, three BSCs are required:



5.5. System-level test

5.5.4. Test Access Port (TAP)

Interface to be included in an IC to support the IEEE 1149 architecture.


Four 1-bit lines (+ optional one) :

- TCK (Test Clock Input). Clock during test.
- TMS (Test Mode Select). Controls test operations
- TDI (Test Data Input). Serial in test data line.
- TDO (Test Data Output). Serial out test data line.

- TRST (Test Reset). TAP controller asynchronous reset optional line.

Architecture

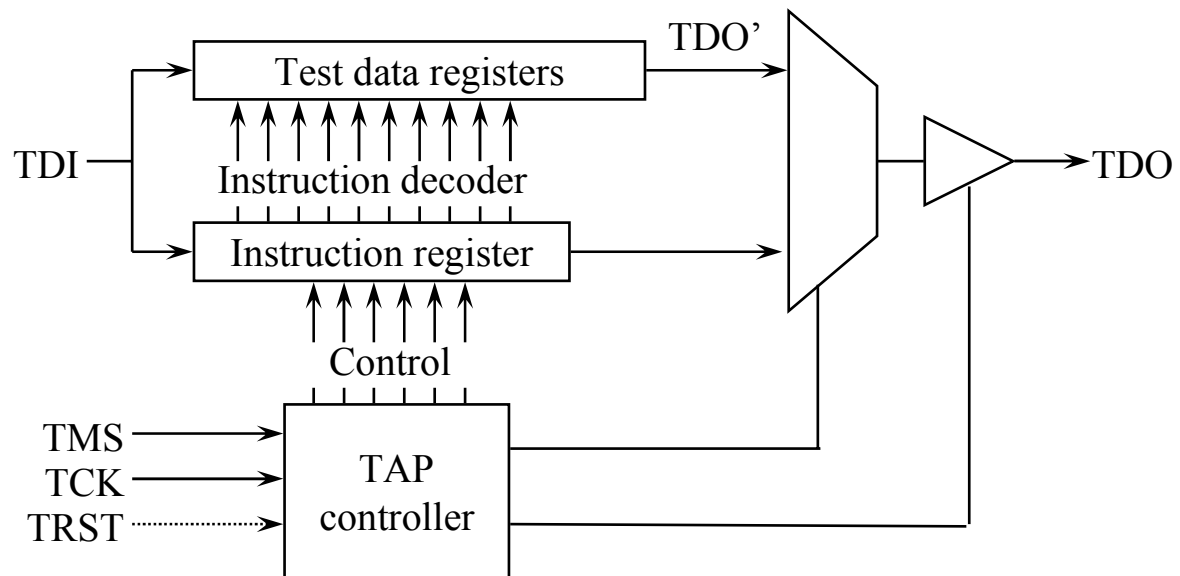- TAP interface pins
- Test data register
- Instruction register
- TAP controller




5.5. System-level test

Test data registers

Transmit test vectors to the combinational circuits and capture the outputs, that are sifted to the serial test data output line (TDO).

They can be:

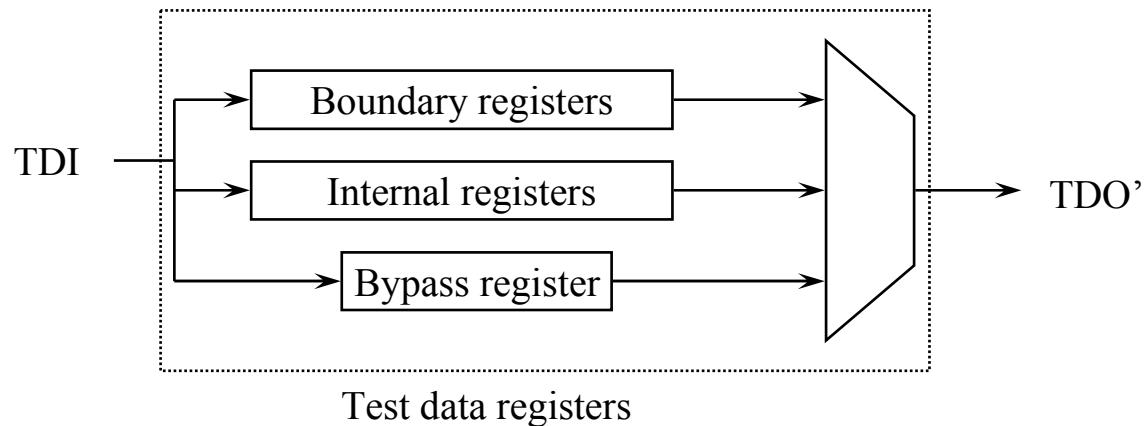- Boundary: Formed by BSCs
- Internal: Internal logic registers
- Bypass (1 bit): Connects TDI to TDO with 1 clock period delay.




5.5. System-level test

TAP controller

16-state Finite State Machine (FSM)

- TCK rising edge transition
- Control variable: TMS

State diagram:

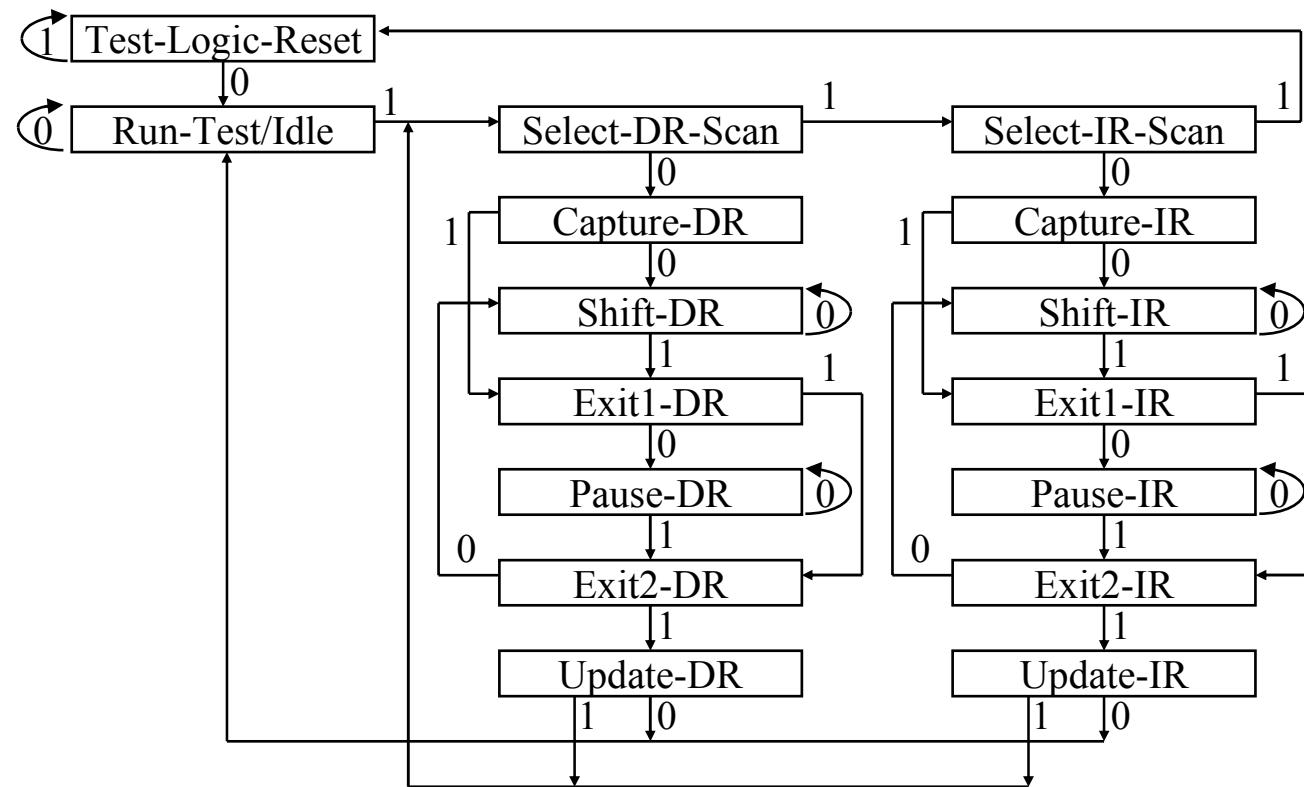

5.5. System-level test

5.5.5. Instruction register

Minimum length: 2 bits.

3 mandatory instructions:

- BYPASS. Code IR = 1...1. Programs IC bypass selecting the bypass 1-bit register. Thus, a system IC can be tested without the delay of the complete test chain.
- EXTEST. Code IR = 0...0. External circuit test.
- SAMPLE/PRELOAD. Selects the boundary registers as a DR chain and preloads or samples IC I/Os.

The following instructions are recommended:

- INTEST. Internal circuits test step through boundary registers.
- RUNBIST. Triggers the IC self-test circuits.

Diagram of one bit of the IR:

