

- **VHDL-based design and synthesis**

- 1. Description of basic primitives**
- 2. Behavioral models of systems**
- 3. The standard synthesis package IEEE Std 1076.3-1997**
- 4. The VHDL RTL synthesis standard IEEE Std 1076.6-1999**

# 1. Description of basic primitives


- **Concurrent assignments and processes:**

➤ **Concurrent assignments:** A change is projected onto the signal placed on the left hand side of the assignment whenever there is a change on the signals placed on the right hand side

$$a \leq b \text{ xor } c;$$


➤ **Processes:** The changes on the signals take place when the is resumed and before its next activation. The activation of a process is a consequence of changes in signals

- **Equivalence:**

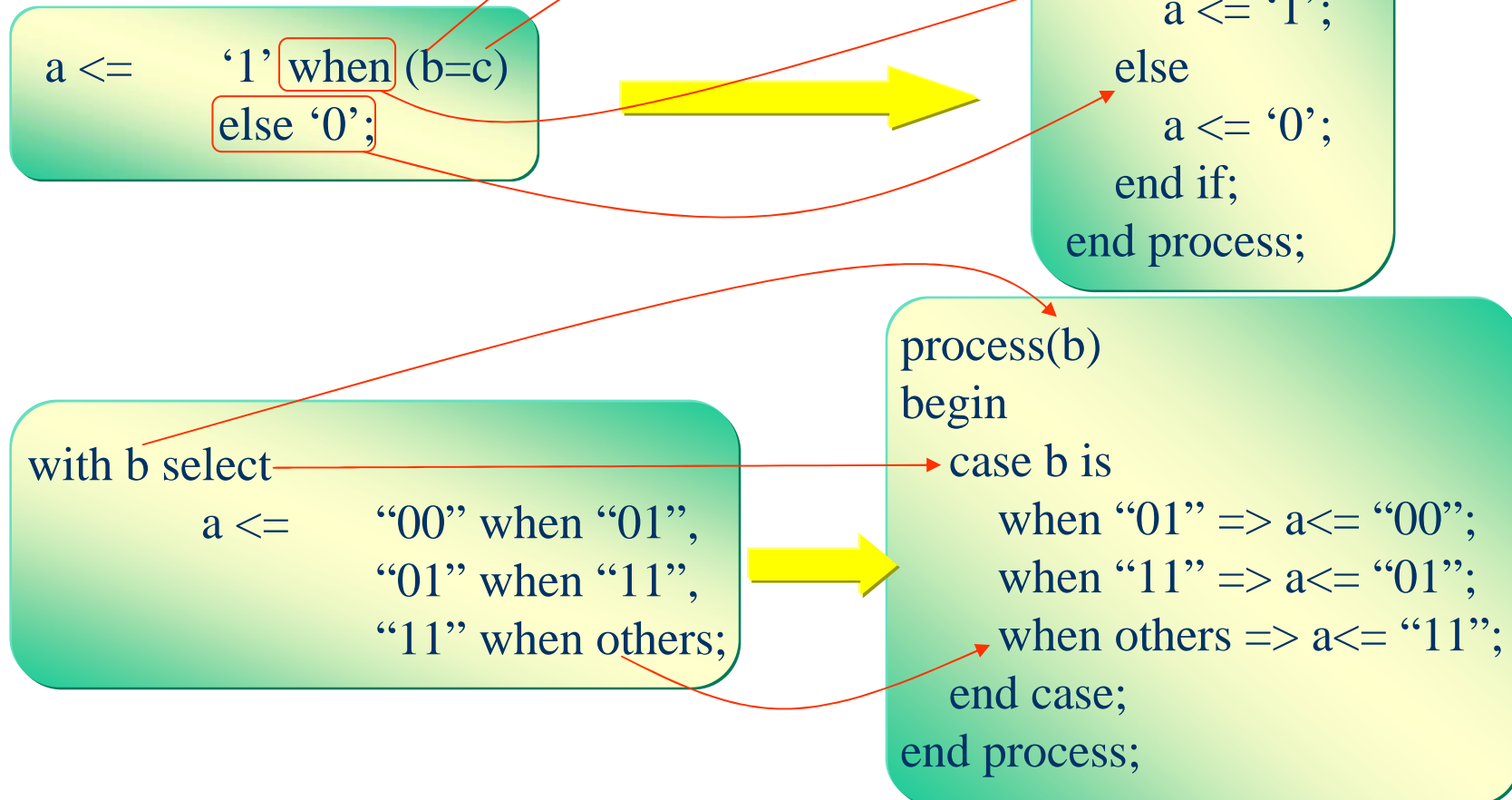

- **Memory on processes:**
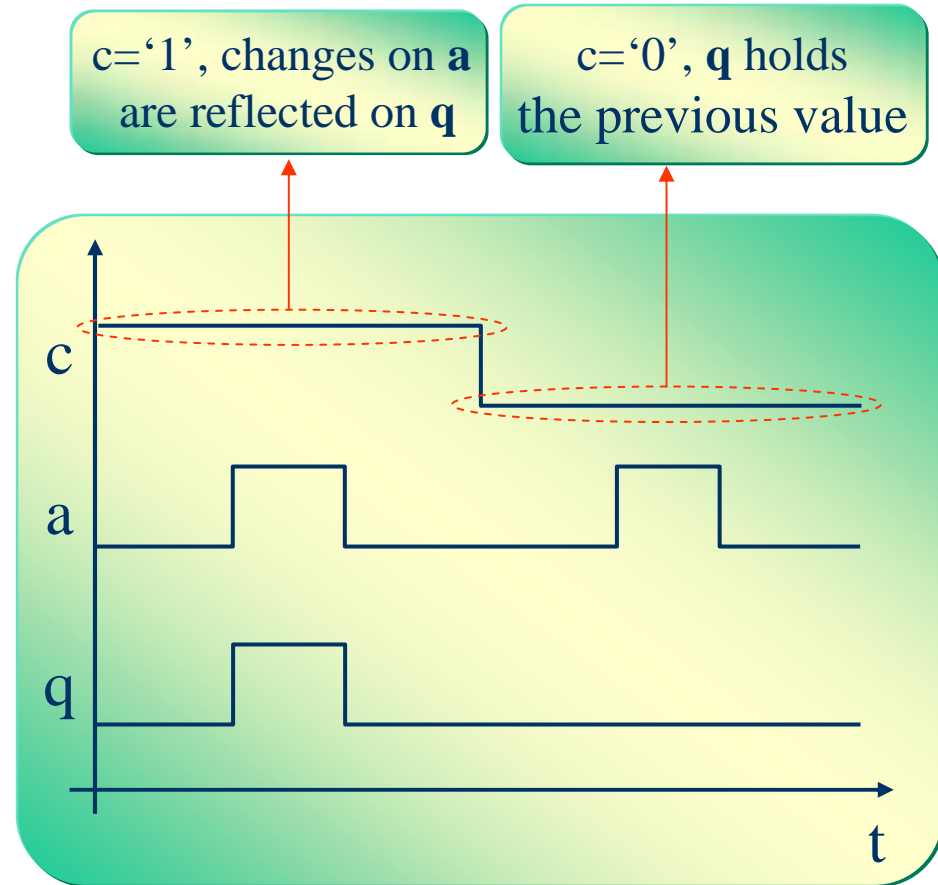
```
process(a,c)
begin
    if (c='1') then
        q <= a;
    end if;
end process;
```



- *General description rules:*

- **Combinational logic:**

- Concurrent assignments (recommended)
- Processes (sensitivity list, default case)

- **Sequential logic:**

- Processes with **wait** primitive  $\Rightarrow$  Flipflops
- Processes with sensitivity list  $\Rightarrow$  Latches

- *Description of combinational logic:*



n m ... b a	f
0 0 ... 0 0	$f_0$
0 0 ... 0 1	$f_1$
0 0 ... 1 0	$f_2$
0 0 ... 1 1	$f_3$
...	
1 1 ... 1 1	$f_n$

```
f <=
  f0 when (n&m&...&b&a="00...00")
  else f1 when (n&m&...&b&a="00...01")
  else f2 when (n&m&...&b&a="00...10")
  else f3 when (n&m&...&b&a="00...11")
  ...
  else fn;
```



```
with (n&m&...&b&a) select
  f <=
    f0 when "00...00",
    f1 when "00...01",
    f2 when "00...10",
    f3 when "00...11",
    ...
    fn when others;
```

- *Feedback in concurrent assignments:*

  
```
control <= a when (enable='1')  
else control;
```


  
```
control <= a when (enable='1')  
else '0';
```



- *Tri-state buffers:*

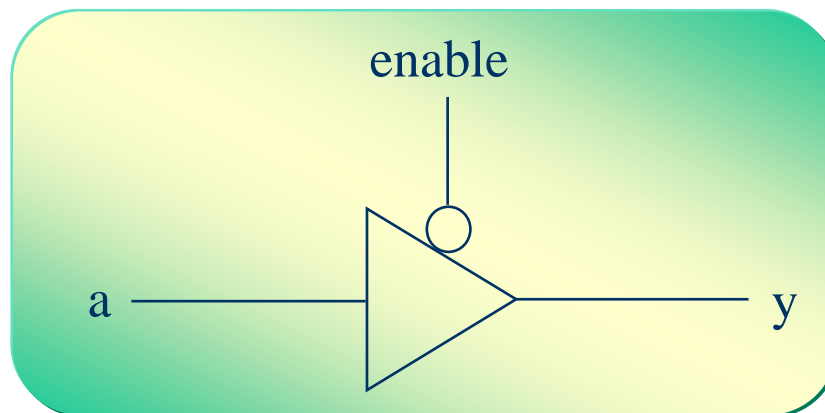

`y <= a when (enable='0')  
else 'Z';`

`std_logic type  
ieee library`



- *Description of sequential logic:*

- **Definition of clock signals:**

- **Wait primitive:**

```
process
begin
    wait until (clk'event and clk='1');
...

```

not clk'stable and clk='1'


- **Sensitivity list (asynchronous control signals):**

```
process(clk)
begin
    if (clk'event and clk='1')
...



```

- *Multiple clock signals:*

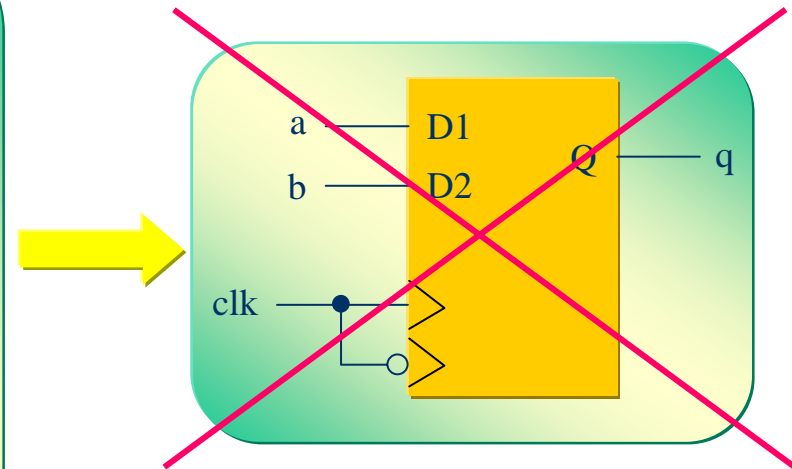
```
m_clock: process(clk)
begin
  if (clk'event and clk='0') then
    q <= a;
  elsif (clk'event and clk='1') then
    q <= b;
  end if;
end process;
```



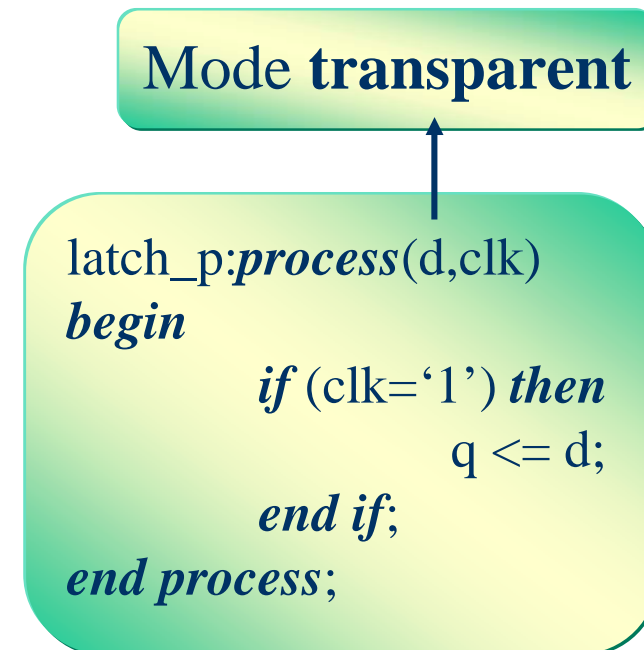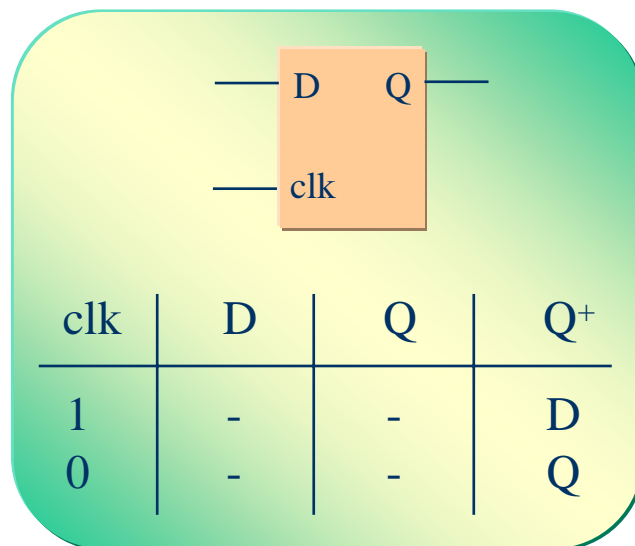- *Sequential primitives active by level (latches):*



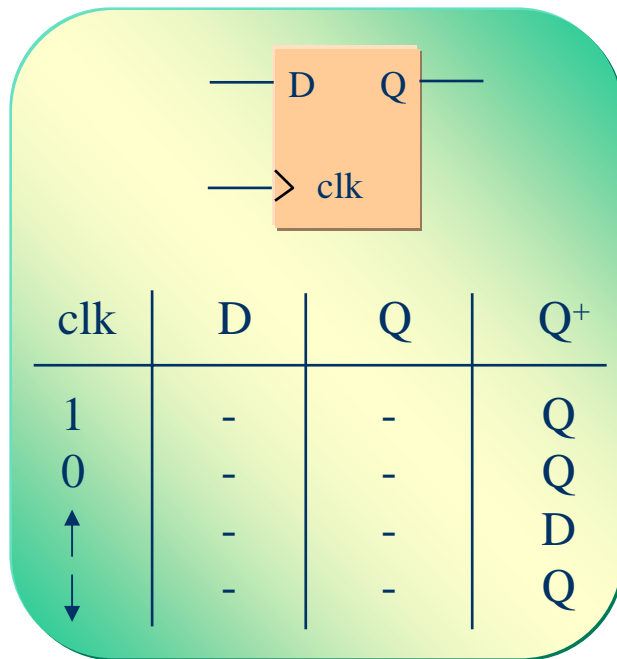- *Sequential primitives active by edge (flipflops):*



*not (clk'stable) and clk='1'*

```

flip_p1: process(clk)
begin
    if (clk'event and clk='1') then
        q <= d;
    end if;
end process;

flip_p2: process
begin
    wait until (clk'event and clk='1');
    q <= d;
end process;

```

- *Control signals:*


### *Asynchronous reset*

```
async_flip: process(clk,clearn)
begin
  if (clearn='0') then
    q <= '0';
  elsif (clk'event and clk='1') then
    q <= d;
  end if;
end process;
```

### *Synchronous reset*


```
sync_flip: process
begin
  wait until (clk'event and clk='0');
  if (clearn='0') then
    q <= '0';
  else
    q <= d;
  end if;
end process;
```

- *E-type register (enable):*

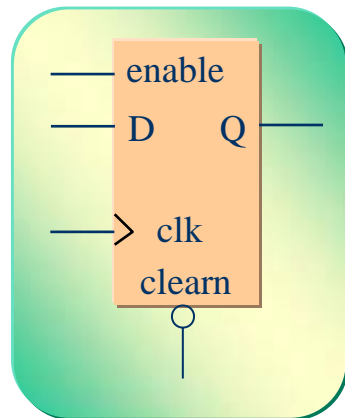


```
E_flipflop: process
begin
    wait until (clk'event and clk='1');
    if (clear='0') then
        Q <= '0';
    elsif (enable='1') then
        Q <= D;
    end if;
end process;
```

- ***T-type register (toggle):***

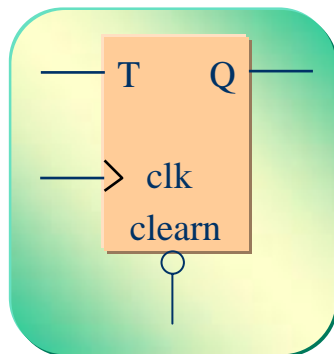

```
T_flipflop: process
begin
  wait until (clk'event and clk='1');
  if (clean='0') then
    Q <= '0';
  elsif (T='1') then
    Q <= not Q;
  end if;
end process;
```

- ***RS-type register (Reset/Set):***

 


```
RS_flipflop: process
begin
    wait until (clk'event and clk='1');
    if (R='1') then
        Q <= '0';
    elsif (S='1') then
        Q <= '1';
    end if;
end process;
```



- *Finite state machines:*

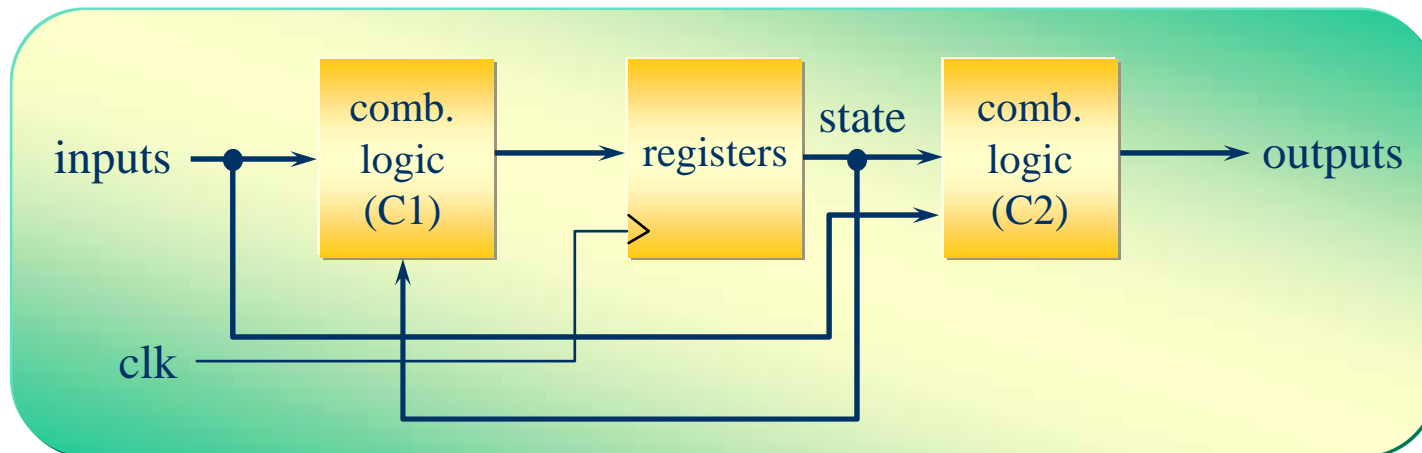- Systems with finite memory (number of states)
- The state of the system and its outputs depend on its previous state and its inputs



- *Structure of a finite state machine:*

architecture description of fsm is

type state is (s0, s1, ..., sn);

signal current\_state, future\_state: state;

begin

**C1** ↓  
future\_state <= s0 when (inputs="..." and current\_state="...")  
                  else s1 when ...  
                  else ...;

registers: process

begin

wait until (clk'event and clk='1');

if (clearn='0') then

    current\_state <= s0;

else


    current\_state <= future\_state;

end if;

end process;

**C2** ↓  
outputs <= "..." when (inputs="..." and current\_state="...")  
          else "..." when ...  
          else ...;

 - **Example:** Detector for the sequence “01”



```

architecture fsm of detector is
  type state is (s0, s1);
  signal current_state, future_state: state;
begin
  future_state <= s0 when (data_in='1')
    else s1;

  registers: process
  begin
    wait until (clk'event and clk='1');
    if (clearn='0') then
      current_state <= s0;
    else
      current_state <= future_state;
    end if;
  end process;
  detect <= '1' when ((current_state=s1) and
    (data_in='1'))
    else '0';
end fsm;
  
```

## 2. Behavioral models of systems

### • Variables vs Signals

#### *Signals*

- Declared in **architecture**
- Assignment **with** delay
- Updated **at the end of a process**
- **Slow** simulation

#### *Variables*


- Declared in **process, block, function, procedure**
- Assignment **without** delay
- Updated **immediately**
- **Fast** simulation

• *If primitive as a priority encoder (I):*

```

process (a,b,c,d,sel)
begin
  if (sel="00") then
    q <= a;
  elsif (sel="01") then
    q <= b;
  elsif (sel="10") then
    q <= c;
  else q <= d;
  end if;
end process;

```

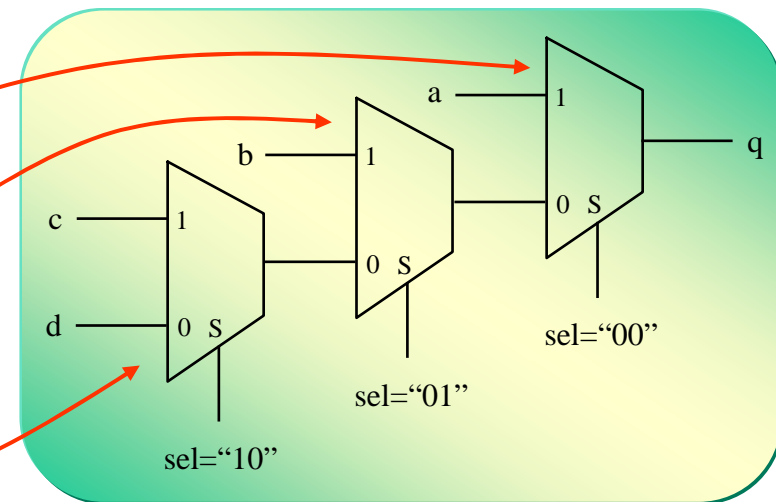


```

q <=  a when (sel="00")
      else b when (sel="01")
      else c when (sel="10")
      else d;

```

- *If primitive as a priority encoder (II):*
 
```
process (a,b,c,d,sel)
begin
    q <= a;
    if (sel="01") then
        q <= b;
    end if;
    if (sel="10") then
        q <= c;
    end if;
    if (sel="11") then
        q <= d;
    end if;
end process;
```




- **Case primitive as a multiplexer:**

```

process (a,b,c,d,sel)
begin
    case sel is
        when "00" => q <= a;
        when "01" => q <= b;
        when "10" => q <= c;
        when others => q <= d;
    end case;
end process;

```

 

- **Case:** Complex decoding
- **If:** Selection with critical delay


```

with sel select
    q <= a when "00",
        b when "01",
        c when "10",
        d when others;


```

- Incomplete decoding:***
 
```
if (clk'event and clk='1')  
    if (req="1000") then  
        q <= d;  
    end if;  
end if;
```


 
```
if (clk'event and clk='1')  
    if (req(3)='1') then  
        q <= d;  
    end if;  
end if;
```






## • Signals with critical delay:

```

if (clk'event and clk='1') then
  if (critica='1' and no_critica='1') then
    o <= in1;
  else
    o <= in2;
  end if;
end if;


```

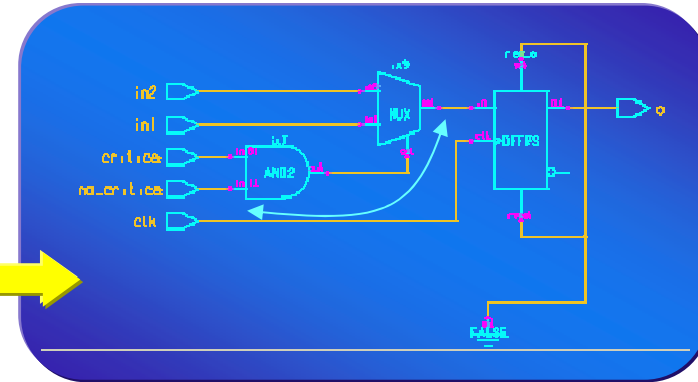

```

if (clk'event and clk='1') then
  if (critica='1') then
    if (no_critica='1') then
      o <= in1;
    else
      o <= in2;
    end if;
  end if;
end if;

```

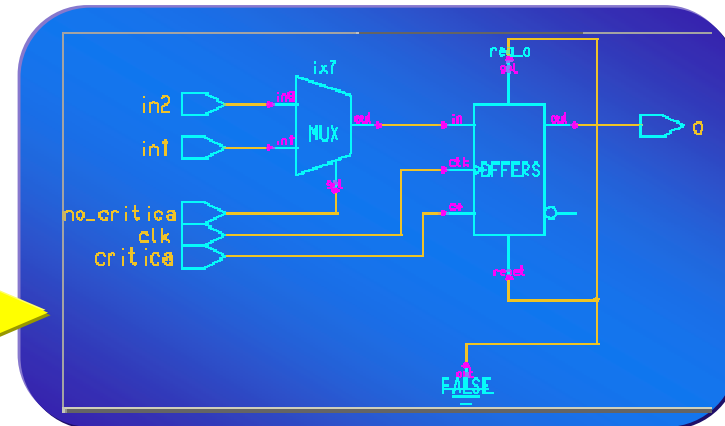


## • Latch inference (I):

```

process(a,b,c,d)
begin
  if (a='1' and b='1' and c='1' and d='1') then
    o <= '1';
  else
    o <= '0';
  end if;
end process;


```

 

```

process(a,b,c,d)
begin
  if (a='1') then
    if (b='1' and c='1' and d='1') then
      o <= '1';
    else
      o <= '0';
    end if;
  end if;
end process;

```

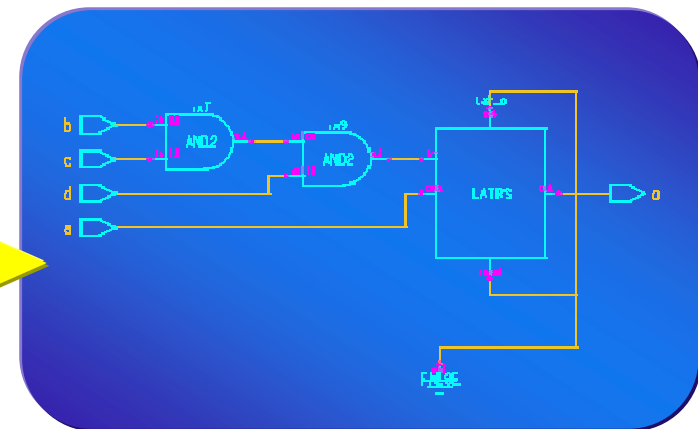


## • Latch inference (II):

```

process(a,b,c,d)
begin
  if (a='1' and b='1' and c='1' and d='1') then
    o <= '1';
  else
    o <= '0';
  end if;
end process;


```

 

```

process(a,b,c,d)
begin
  if (a='1') then
    if (b='1' and c='1' and d='1') then
      o <= '1';
    end if;
  else
    o <= '0';
  end if;
end process;

```


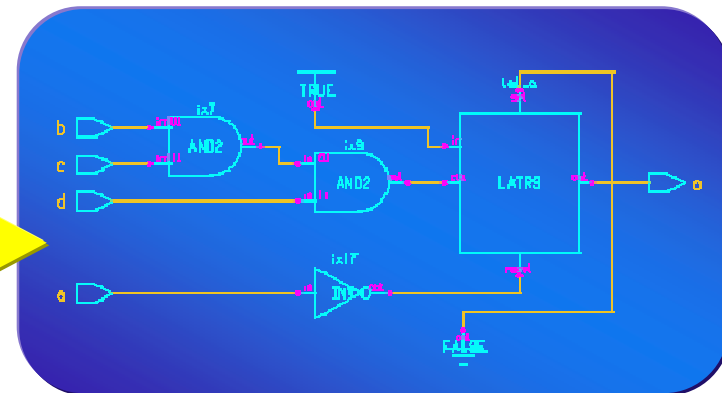


## • Priority for critical signals (I):

```

process(a,b,c,d)
begin
  if (a='1' and b='1' and c='1' and d='1') then
    o <= '1';
  else
    o <= '0';
  end if;
end process;


```

  

```

process(a,b,c,d)
begin
  if (a='1') then
    if (b='1' and c='1' and d='1') then
      o <= '1';
    else o <= '0';
    end if;
  else
    o <= '0';
  end if;
end process;

```

 


## • Priority for critical signals (II):

```

process(a,b,c,d)
begin
  if (a='1' and b='1' and c='1' and d='1') then
    o <= '1';
  else
    o <= '0';
  end if;
end process;


```

 

```


process(a,b,c,d)
begin
  if (a='1' and (b='1' and c='1' and d='1')) then
    o <= '1';
  else
    o <= '0';
  end if;
end process;

```

 


- **Resource sharing:**
 
```
if (sel)
    q <= a+b;
else
    q <= c+d;
end if;
```



 
```
if (sel)
    op1 <= a;
    op2 <= b;
else
    op1 <= c;
    op2 <= d;
end if;
q <= op1+op2;
```



- ***Scheduling of operations:***

- sel1, sel2 mutually exclusive
 
```
if (sel1) then
    q <= a+b;
elsif (sel2) then
    q <= a+c;
end if;
```




- 1 control level
- 1 adder

```
if (sel1) then
    q <= a+b;
else
    if (sel2) then
        q <= a+c;
    end if;
end if;
```



 - 1-2 control levels
- 1 adder

```
if (sel1) then
    q <= a+b;
end if;
if (sel2) then
    q <= a+c;
end if;
```



- 3-4 control levels
- 1-2 adders




## • Operations inside loops:

```

for i in 0 to 3 loop
  if (sel(i)='1') then
    q <= a + offset(i);
  end if;
end loop;


```

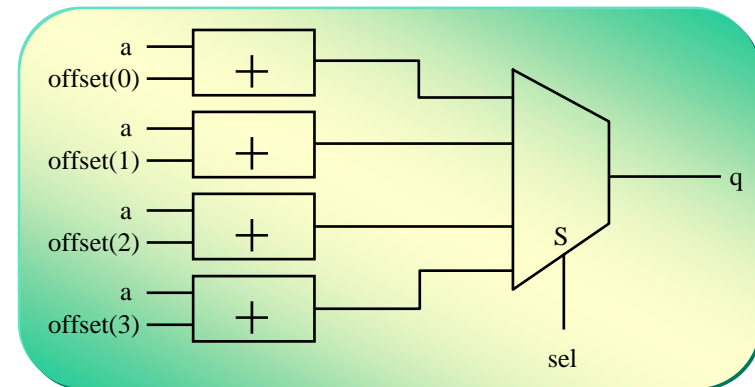

```

for i in 0 to 3 loop
  if (sel(i)='1') then
    add_offset <= offset(i);
  end if;
end loop;
q <= a+add_offset;


```

 




- **Loop expansion:**

 
```
q <= initial_value;  
for i in 0 to 2 loop  
  q <= q+inc(i);  
end loop;
```


 
```
q <= ((initial_value+inc(0)) +  
      (inc(1)+inc(2)));
```



• **FPGAs:**

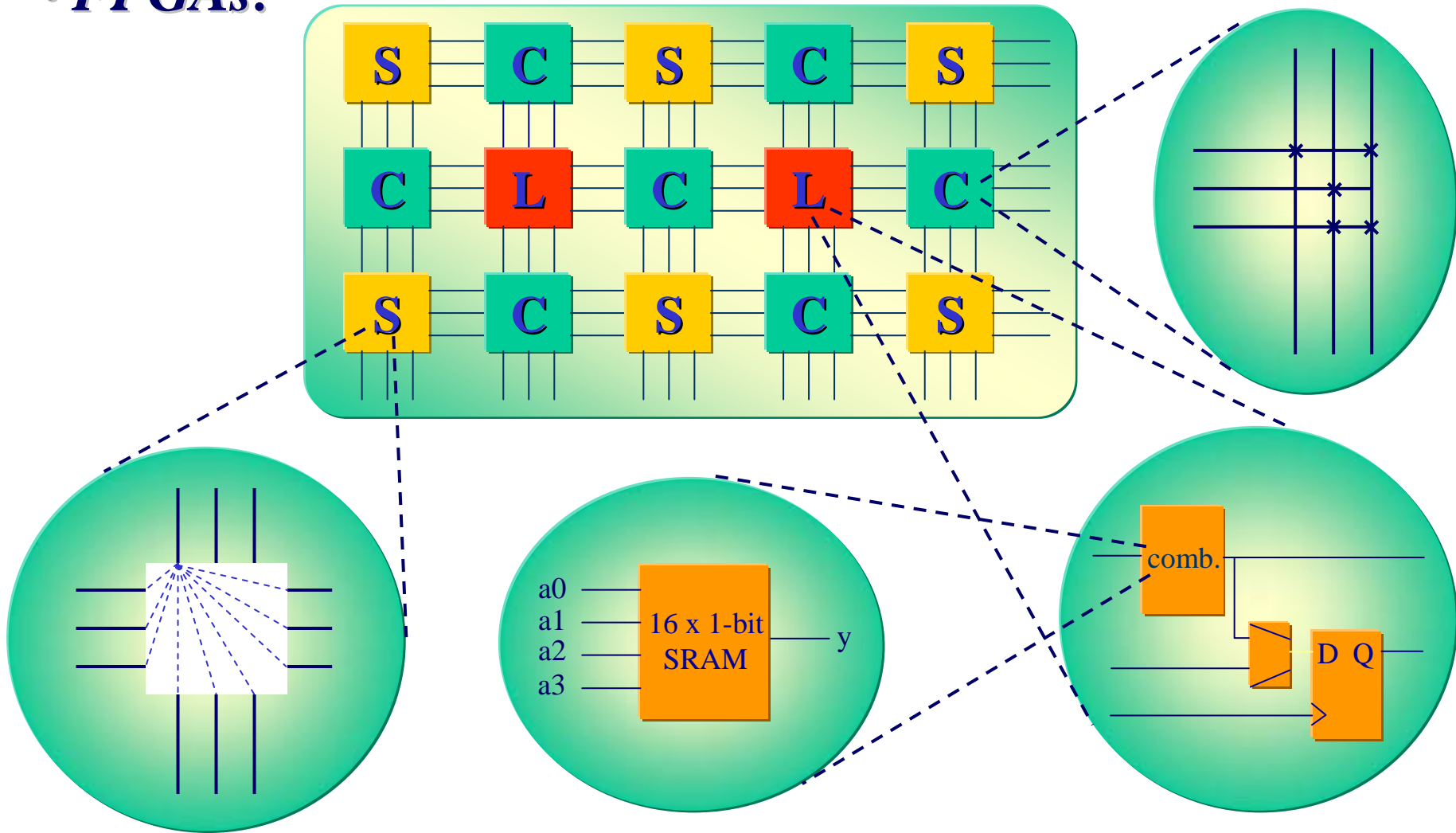

- *Synthesis principles for FPGAs:*

- **Limited resources:**

- combinational elements
- sequential elements
- connectivity

- **Execution delay:**

$$t_{total} = t_{component} + t_{routing} + t_{switch}$$

$t_{routing}, t_{switch} \gg t_{component}$ , and  
unknown before the physical design (P & R)

Values to  
minimise

- ***Minimisation of the connectivity delay:***

- **Use specific hardware macros:**

- Adders / subtractors

- Shifters / rotators

- Counters

- Shift registers

- Memory blocks

- **One-hot encoding for finite state machines**

### 3. The standard synthesis package IEEE 1076.3-97

- Interpretation for synthesis of the types *BIT*, *BOOLEAN* and *STD\_ULOGIC*
- Definition of the function *STD\_MATCH*
- Definition of functions to handle signal edges
- Definition of function for representing signed and unsigned values, as well as conversion functions between types

➤ **type** `STD_ULOGIC` is ('1', '0', 'H', 'L', 'U', 'X', 'W', '-', 'Z');

The diagram illustrates the mapping of characters in the `STD_ULOGIC` type. A vertical red arrow points from the character '1' to the text 'resolved', which is positioned above the text 'STD\_LOGIC'. Two horizontal red lines are drawn under the characters 'H', 'L', 'U', and 'X'. From the center of the first line, a red arrow points down to the text 'logical values'. From the center of the second line, a red arrow points down to the text 'metalogical values'.

- **Interpretation of logical values:**
  - **Interpretation as a value 0:**
    - The value '0' of type BIT
    - The value FALSE of type BOOLEAN
    - The values '0' and 'L' of type STD\_ULOGIC
  - **Interpretation as a value 1:**
    - The value '1' of type BIT
    - The value TRUE of type BOOLEAN
    - The values '1' and 'H' of type STD\_ULOGIC
- **Interpretation of metalogical values:**
  - **Relational expressions:** In an equality relation, if one operand is a metalogical value and the other is not a static value, the result should be the value FALSE

- **Interpretation of metalogical values:**
  - **Case primitives:** If a metalogical value occurs in a choice, the synthesis tool shall interpret the choice as one that can never occur
  - **Arithmetic, logic and shift operations:** The synthesis tool shall treat the operation as an error
  
- **Interpretation of the high impedance ('Z') value:**
  - If the value 'Z' occurs in an assignment, the synthesis tool shall convert the assignment in a tri-state buffer
  - If the value 'Z' occurs in any construction different from an assignment, the synthesis tool shall treat it as a metalogical value

- **The STD-MATCH function:**

- If this function is applied to two arguments of type STD\_ULOGIC, it will return the TRUE value if:
  - Both values are well-defined and are the same, or
  - One value is '0' and the other is 'L', or
  - One value is '1' and the other is 'H', or
  - At least one of the values is '-'
- If this function is applied to two arguments that are vectors of type STD\_ULOGIC, it will return the TRUE value if:
  - The operands have the same length, and
  - STD\_MATCH applied to each pair of matching elements returns TRUE

- **Edge detection:** *rising\_edge(signal)*, *falling\_edge(signal)*



- **Standard arithmetic packages:**
  - **NUMERIC\_BIT:** Based on the BIT type
  - **NUMERIC\_STD:** Based on the STD\_LOGIC type
- **New types:**

- **UNSIGNED:** Unsigned integer, with the most significant bit on the left
- **SIGNED:** Integer in 2's complement, with the most significant bit on the left

## 4. The VHDL RTL synthesis standard IEEE 1076.6-1999

- Approved on July de 1998 (IEEE Std 1076.6-1999)
- Motivation for VHDL: Modelling of electronic systems


*Syntactic and semantic flexibility*

- Impossible to cover the whole language
- Tool-dependent synthesis

*Non-portable  
synthesis*

- **Motivation for a standard synthesis subset:**

- **Portability between tools**

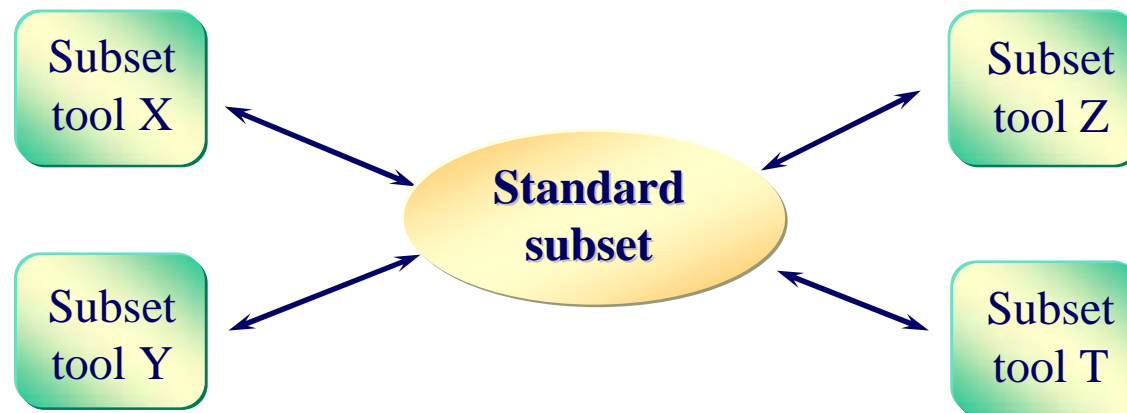

- **Design portability (specification language):**



- ***The VHDL RTL synthesis standard (IEEE 1076.6)***

- **RTL description:**

- Data transfer between memory elements (registers)
- Combinational logic

- **Supported data types:**

- BIT, BOOLEAN, BIT\_VECTOR, CHARACTER, STRING, INTEGER (1076-2000)
- STD\_ULOGIC, STD\_ULOGIC\_VECTOR, STD\_LOGIC, STD\_LOGIC\_VECTOR (1164-1993)
- SIGNED, UNSIGNED (1076.3-97)

- ***Sequential primitives active by edge (flipflops):***
  - **Clock signal:** Types BIT, STD\_ULOGIC, STD\_LOGIC
  - **Specification of a clock (rising) edge:**

- **With the *if* statement:**
  - **rising\_edge(clock)**
  - **clock'event and clock='1'**
  - **clock='1' and clock'event**
  - **not clock'stable and clock='1'**
  - **clock='1' and not clock'stable**

➤ **Specification of a clock (rising) edge:**

• **With the *wait until* statement:**

- **rising\_edge**(clock)
- clock='1'
- clock'**event** and clock='1'
- clock='1' and clock'**event**
- **not** clock'**stable** and clock='1'
- clock='1' and **not** clock'**stable**

➤ **Only one clock edge per process** is allowed

➤ The **wait until** is not allowed within procedures

## • Modelling:

```
process(clock)
begin
  if (clock'event and clock='1') then
    q <= d;
  end if;
end process;
```

```
process
  variable var: unsigned(3 downto 0);
begin
  wait until (clock = '1');
  var := var + 1;
  count <= var;
end process;
```

```
process
begin
  wait until (clock='1');
  q <= d;
end process;
```

- **One** per process
- **First** statement

Variable read before  
being assigned

- **Asynchronous control signals:**

```
process(clk, set, reset)
begin
    if (reset='1') then
        Q <= '0';
    elsif (set='1') then
        Q <= '1';
    elsif (clk'event and clk='1') then
        Q <= D;
    end if;
end process;
```



- *Sequential primitives active by level (latches):*

- **Necessary inference:**

- One signal or variable is assigned in a process without definition of clock signals **and**
- There are executions of the process that do not imply an explicit assignment on the signal or variable

- **Probable inference:**

- One signal or variable is assigned in a process without definition of clock signals **and**
- There are executions of the process where the value of the signal or variable is read before it is assigned

- **Tri-state buffers:** Conditional assignment of the value 'Z' on a signal or variable

- **Modelling of combinational logic:**

- Concurrent assignments
- Assignments within a process that take place with every execution of the process

- **Meta-comments:**

```
-- RTL_SYNTHESIS ON  
-- RTL_SYNTHESIS OFF
```

- **ENUM\_ENCODING attribute:** Used to instruct the synthesis tools the coding to be used for the elements that constitute an enumerated type (finite state machines)

```
attribute ENUM_ENCODING: string;
```

```
type state is (s0, s1, s2, s3);
```

```
attribute ENUM_ENCODING of state: type is  
"0001 0010 0100 1000";
```