

## Application and Design Examples


### 3 Application and design examples

#### 3.1 Switching off inductive loads

The discharge of an inductor produces high voltages that endanger both the contact breaker (switching transistor and the like) and the inductor itself. According to equation 16 the energy stored in the coil is  $\frac{1}{2} L i^2$ . So, when the inductor is switched off, this energy charges a capacitor in parallel with the inductor (this capacitor can also be the intrinsic capacitance of the coil). Not allowing for the losses, and for  $\frac{1}{2} C v^2 = \frac{1}{2} L i^2$ , the values of figure 23 produce:

$$v^* = i^* \sqrt{\frac{L}{C}} = 1 \sqrt{\frac{0,1}{250 \cdot 10^{-12}}} = 20\,000 \text{ V}$$

 To suppress this transient, a varistor is to be connected in parallel with the inductor as a fly-wheel circuit.



$V_{DC}$	= 24 V
$L$	= 0,1 H
$R_{Cu}$	= 24 $\Omega$
$I$	= 1 A
$C$	= 250 pF

Required switching rate	= $10^6$
Period	= 10 s
Required protection level	< 65 V

**Figure 23** Limiting switching transients with a varistor as fly-wheel circuit

#### Operating voltage

The DC operating voltage is given as 24 V (cf. figure 23). If the possible increase in operating voltage is no more than 2 V, types with a maximum permissible DC operating voltage of 26 V should be chosen from the product tables to arrive at as low a protection level as possible. The types available in this category are

– disks	S...K20
– SMDs	CU....K20G2, CN....K20G
– hicaps	SR.K20M...

## Application and Design Examples

---

### Surge current

When it is cut off, the current through an inductor cannot change abruptly, so it flows across the varistor initially with the value of the operating current (here 1 A), then decaying towards zero following an exponential function.

The simplest ways of determining the current duration are simulation or measurement ( $\tau = t_r^*$ ).

The time constant can also be calculated to an approximation with equation 13.

Here the varistor resistance of voltage class K20 is calculated for 1 A. As the protection levels of the various type series do not differ much, the S10K20 has been chosen arbitrarily to determine the resistance (the voltage is taken from the appropriate  $V/I$  characteristics).

$$R_{SIOV} = \frac{55 \text{ V}}{1 \text{ A}} = 55 \Omega$$

So  $\tau$  according to equation 13 is

$$\tau = t_r^* = \frac{0,1 \text{ H}}{24 \Omega + 55 \Omega} \approx 1,3 \text{ ms}$$

For S10K20 with  $t_r^* = 1,3 \text{ ms}$  and  $10^6$  load repetitions, one can derive

$$i_{\max} = 3 \text{ A} > i^* = 1 \text{ A}$$

from the derating curves.

Taking this result, one should check whether other types with lower current ratings satisfy the selection criterion:

$$\text{S05K20: } i_{\max} = 0,5 \text{ A} < i^* = 1 \text{ A}$$

$$\text{S07K20: } i_{\max} = 1,4 \text{ A} > i^* = 1 \text{ A}$$

So the selection criterion of equation 9 is met by SIOV-S07K20 and all types with higher current ratings.

If an SMD is to be used, this can be selected from either the SIOV-CU or SIOV-CN ranges.

SIOV-CU: CU4032K20G2 is the electrical equivalent of S07K20.

SIOV-CN: CN1206K20G, with  $i_{\max} = 1,5 \text{ A} > i^* = 1 \text{ A}$  fulfills the selection criteria.

### Energy absorption

The maximum energy absorption capacity of SIOV-S07K20 for  $t_r^* = 1,3 \text{ ms}$ ,  $i_{\max} = 1,4 \text{ A}$  and  $10^6$  repetitions according to equation 17 is

$$W_{\max} = V_{\max} \cdot i_{\max} \cdot t_{r \max} = 60 \cdot 1,4 \cdot 0,0013 = 0,11 \text{ J (with } t_{r \max} = t_r^* \text{ according to 2.5.3)}$$

According to equation 16 the varistor must in the worst case absorb an energy of

$$W^* = 1/2 L i^{*2} = 1/2 \cdot 0,1 \text{ H} \cdot 1 \text{ A}^2 = 0,05 \text{ J} < W_{\max} = 0,11 \text{ J}$$

per switching cycle. Thus SIOV-S07K20 and CU4032K20G2 also satisfy the selection requirement of equation 10.

For CN1206K20G the result is  $W_{\max} = 58 \cdot 1,5 \cdot 0,0013 = 0,11 \text{ J} > 0,05 \text{ J}$ .

This varistor is therefore also suitable.

### *Average power dissipation*

According to equation 18, applied energy of 0,05 J every 10 s produces an average power dissipation of

$$P^* = \frac{W^*}{T^*} = \frac{0,05}{10} = 0,005 \text{ W}$$

The product table shows a maximum dissipation capability of 0,02 W for SIOV-S07K20 and CU4032K20G2. So on this point too, the choice is correct (equation 11).

For the sake of completeness, the minimum permissible time between two applications of energy is calculated (equation 19):

$$T_{\min} = \frac{W^*}{P_{\max}} = \frac{0,05 \text{ J}}{0,02 \text{ W}} = 2,5 \text{ s}$$

For CN1206K20G, with  $P_{\max} = 0,008 \text{ W}$  the result is

$$T_{\min} = \frac{W^*}{P_{\max}} = \frac{0,05 \text{ J}}{0,008 \text{ W}} = 6,2 \text{ s}$$

### *Maximum protection level*

The *V/I* curve for S07K20 and/or CU4032K20G2 shows a protection level of 60 V at 1 A for the worst case position in the tolerance field (PSpice supplied by S+M: TOL = +10).

The protection level for CN1206K20G is 55 V.

This means that all three types meet the requirement for a protection level < 65 V.

The hicap varistors SHCV-SR.K20... also satisfy all the selection criteria. Their use can have a positive effect as far as contact erosion and RFI are concerned. They also mean a reduction of the maximum protection level to 50 V.

## 3.2 CE conformity

A wide range of legislation and of harmonized standards have come into force and been published in the field of EMC in the past few years. In the European Union, the EMC Directive 89/336/EEC of the Council of the European Communities has come into effect on the 1st of January 1996. As of this date, all electronic equipment must comply with the protective aims of the EMC Directive. The conformity with the respective standards must be guaranteed by the **manufacturer or importer** in the form of a declaration of conformity. A CE mark of conformity must be applied to all equipment [1].

As a matter of principle, all electrical or electronic equipment, installations and systems must meet the protection requirements of the EMC Directive and/or national EMC legislation. A declaration of conformity by the manufacturer or importer and a CE mark are required for most equipment. Exceptions to this rule and special rulings are described in detail in the EMC laws.

---

[1] Kohling, Anton "CE Conformity Marking"  
ISBN 3-89578-037-5, Ordering code: A19100-L531-B666

## Application and Design Examples

---

New, harmonized European standards have been drawn up in relation to the EEC's EMC Directive and the national EMC laws. These specify measurement techniques and limit values or severity levels, both for interference emission and for the interference susceptibility (or rather, immunity to interference) of electronic devices, equipment and systems.

The subdivision of the European standards into various categories (cf. table 1) makes it easier to find the rules that apply to the respective equipment.

The generic standards always apply to all equipment for which there is no specific product family standard or dedicated product standard.

Adherence to the standards for electromagnetic compatibility (EMC) is especially important.

These are:

- Interference emission EN 50081
- Immunity to interference EN 50082

Whereas regulations concerning maximum interference emission have been in existence for some time, binding requirements concerning immunity to interference have only come into existence since 1996 for many types of equipment. In this respect, in addition to having an optimum price/performance ratio, SIOV varistors have proved themselves to be a reliable solution for all requirements concerning overvoltages:

- ESD (electrostatic discharge)
- Burst (fast transients)
- Surges, high-energy transients

The basic standards contain information on interference phenomena and general measuring methods.

The following standards and regulations form the framework of the conformity tests:

**Table 1**

EMC standards	Germany	Europe	International
---------------	---------	--------	---------------

### Generic standards

define the EMC environment in which a device is to operate according to its intended use

Emission	residential	DIN EN 50081-1	EN 50081-1	—
	industrial	DIN EN 50081-2	EN 50081-2	—
Susceptibility	residential	DIN EN 50082-1	EN 50082-1	—
	industrial	DIN EN 50082-2	EN 50082-2	—

**Table 1** (continued)

EMC standards	Germany	Europe	International
<b>Basic standards</b>			
describe physical phenomena and measurement techniques			
Basic principles	DIN VDE 0843	EN 61000	IEC 1000
Measuring equipment	DIN VDE 0876		CISPR 16-1
Measuring methods	DIN VDE 0877	EN 61000-4-1	CISPR 16-2 IEC 1000-4-1
Harmonics	DIN VDE 0838	EN 60555-2	IEC 1000-3-2
Interference factors			
e. g.	ESD	EN 61000-4-2	IEC 1000-4-2
	EM fields	EN 61000-4-3	IEC 1000-4-3
	Burst	EN 61000-4-4	IEC 1000-4-4
	Surge	EN 61000-4-5	IEC 1000-4-5

## Product standards

define limit values for emission and susceptibility

EMC standards	Germany	Europe	International
ISM equipment <sup>2)</sup>	DIN VDE 0875 T11 1)	EN 55011 1)	CISPR 11 1)
Household appliances	DIN VDE 0875 T14-1 DIN VDE 0875 T14-2	EN 55014-1 EN 55014-2	CISPR 14-1 CISPR 14-2
Lighting	DIN VDE 0875 T15-1 DIN VDE 0875 T15-2	EN 55015-1 EN 55015-2	CISPR 15 IEC 3439
Radio and TV equipment	DIN VDE 0872 T13 DIN VDE 0872 T20	EN 55013 EN 55020	CISPR 13 CISPR 20
High-voltage systems	DIN VDE 0873	EN 55018	CISPR 18
IT equipment <sup>3)</sup>	DIN VDE 0878 DIN VDE 0878	EN 55022 EN 55022	CISPR 22 CISPR 22
Vehicles	DIN VDE 0879 DIN VDE 0839	EN 72245	CISPR 25 ISO 11451/S2

1) Is governed by the safety and quality standards of the product families

2) Industrial, scientific and medical devices and equipment

3) Information technology facilities

## Application and Design Examples

**Table 1** (continued)

The following table shows the most important standards in the field of immunity to interference.

Standard	Test characteristics	Phenomena
<b>Conducted interference</b>		
EN 61000-4-4 IEC 1000-4-4	5/50 ns (single pulse) 15 kHz burst	Burst Cause: switching processes
EN 61000-4-5 IEC 1000-4-5	1,2/50 $\mu$ s (open-circuit voltage) 8/20 $\mu$ s (short-circuit current)	Surge (high-energy transients) Cause: lightning strikes mains lines, switching processes
EN 61000-4-6 (ENV 50141) IEC 801-6	1 V, 3 V, 10 V 150 kHz to 80 MHz	High-frequency coupling Narrow-band interference
<b>Field-related interference</b>		
EN 61000-4-3 (ENV 50140) IEC 801-3	3 V/m, 10 V/m 80 to 1000 MHz	High-frequency interference fields
<b>Electrostatic discharge (ESD)</b>		
EN 61000-4-2 IEC 1000-4-2	Up to 15 kV figure 24	Electrostatic discharge

The IEC 1000 or EN 61000 series of standards are planned as central EMC standards into which all EMC regulations (e. g. IEC 801, IEC 555) are to be integrated in the next few years.

### 3.2.1 ESD


The trend to ever smaller components and lower and lower signal levels increases the susceptibility of electronic circuits to interference due to electrostatic disturbances. Simply touching the device may lead to electrostatic discharge causing function disturbances with far-reaching consequences or to component breakdown. Studies have shown that the human body on an insulated ground surface (e. g. artificial fiber carpeting), can be charged up to 15 kV.

In order to safeguard the immunity to interference and thus ensure CE conformity, measures are needed to prevent damage due to electrostatic discharge (ESD). This applies to both the circuit layout and to selection of suitable overvoltage protection.


EN 61000-4-2 describes the test procedures and specifies severity levels:

Figure 24 shows the discharge circuit, figure 25 the waveform of the discharge current with an extremely short rise time of 0,7 to 1,0 ns and amplitudes of up to 45 A. Secondary effects caused by this edge steepness are high electrical and magnetic fields strengths.

In the ESD test, at least 10 test pulses of the polarity to which the device under test is most sensitive are applied.

 

**Figure 24** ESD discharge circuit according to EN 61000-4-2

 

**Figure 25** ESD discharge current according to EN 61000-4-2

For this reason, suitable overvoltage protection elements must meet the following requirements:

- response time < 0,5 ns
- bipolar characteristics
- sufficient surge current handling capability
- low protection level

## Application and Design Examples

---

In addition, the following requirements are desirable:


- smallest possible component size
- SMD design
- high capacitance values for RF interference suppression, or low capacitance values for systems with high-speed data transmission rates, respectively
- wide operating voltage range
- high operating temperature

All these requirements are optimally fulfilled by SIOV multilayer varistors (CN series). The extremely low inductance of their construction reduces the response time to  $< 0,5$  ns. Consequently, in order to utilize this advantage to the full, the lowest possible connection inductance is required.

The fields of application are, in particular:

- cordless and cellular phones ("handies")
- SCART sockets
- data transmission lines
- interfaces such as RS232, CENTRONICS
- PC (keyboard, mouse, printer ports etc.)
- LANs, modems, sensors
- interface circuits

Often, for example in SCART sockets of TV sets and video recorders, signal lines are connected with two Z diodes in serial and opposing polarity and a decoupling capacitor. Replacing these three components by a multilayer varistor leads to considerable cost and space savings (figure 26).

 

**Figure 26** A multilayer varistor can replace three components

The adaptation to the capacitance values of the decoupling capacitor can be achieved by correct selection of the model and/or the voltage class:

- higher capacitance values are achieved by selecting a larger model,
- lower capacitance values are achieved by selecting a smaller model, or, where this is not possible, a higher voltage class.



## Application and Design Examples

---

### 3.2.2 Energy of an ESD pulse

EN 61000-4-2 specifies 15 kV as the highest charging voltage (severity level 4, air discharge) for the 150 pF discharge capacitor according to figure 24.

This means that the stored energy is

$$W^* = 0,5 \cdot C \cdot V^2 = 0,5 \cdot 150 \cdot 10^{-12} \cdot 15^2 \cdot 10^6 < 0,02 \text{ J}$$

The 330-Ω resistor limits the surge current to a maximum of

$$\hat{i}^* = \frac{V^*}{R} = \frac{15\,000 \text{ [V]}}{330 \text{ [Ω]}} \approx 45 \text{ A}$$

If this surge current is to be handled by a multilayer varistor, then, according to equation 12, the effect of the varistor on this value of the current amplitude is negligible.

For CN0805M6G, for example, this means that:

$$\hat{i}^* = \frac{V_s - V_{\text{SIOV}}}{Z_{\text{source}}} = \frac{15\,000 \text{ [V]} - 45 \text{ [V]}}{330 \text{ [Ω]}} \approx 45 \text{ A}$$

By transforming the discharge current (figure 25) into an equivalent rectangular wave, we obtain  $t_r^* \approx 40 \text{ ns}$ .

No value can be deduced from the derating curves for such an extremely short current flow time.

The energy absorption of multilayer varistors during ESD discharges lies in the region of μJ.

For the SIOV-CN0805M6G, for example, according to equation 15 this means that:

$$W^* = \hat{v}^* \hat{i}^* t_r^* = 45 \cdot 45 \cdot 40 \cdot 10^{-9} = 80 \text{ μJ}$$

Thus one can expect the largest part of the energy content of the ESD pulse to be absorbed by the 330-Ω discharge resistor.

If EN 61000-4-5 (surge voltage) is taken into consideration when selecting the varistor, it can be assumed that, where applicable, ESD specifications are also covered by the varistor. Due to the steep edge of the ESD pulse, the mechanical construction of a device is of great importance for the test result. The ESD varistor selection should therefore always be verified by a test circuit.

### 3.2.3 Burst

According to EN61000-4-4 (IEC 1000-4-4), burst pulses are low-energy transients with steep edges and high repetition rate. Thus, for equipment to pass burst testing successfully, design and construction are as critical as the choice of the varistor. If EN 61000-4-5 has been taken into account when selecting varistors, they will normally also handle the burst pulse energy without any problems. Due to the steepness of the pulse edges, the varistors must be connected in a way which keeps parasitic circuit inductance low. Our EMC laboratory in Regensburg will carry out tests on request (cf. 3.2.6).

### 3.2.4 Surge voltages

The immunity to interference against (high-energy) surge voltages is tested in accordance with EN 61000-4-5 (IEC 1000-4-5). The overvoltage is generated using a hybrid generator such as specified in EN 61000-4-5 and is then coupled in via the individual leads of the device under test.

The severity level of the test (i.e. the charging voltage and thus the energy content) is defined in relation to the installation conditions. In most cases, the respective product standards demand 5 positive and 5 negative voltage pulses.

Varistors suitable for 230 V and 400 V mains are given in tables 2a and 2b, in each case as a function of the required severity levels and the source impedance. An impedance of 2 Ω is used in the line-to-line test.

12 Ω is specified for the line-earth test:

The tables show that smaller components may be used.

**Note:**

Connection of varistors to earth may be subject to restrictions. This must be clarified with the respective authorization offices.

For all lines which do not serve to supply electricity, EN 61000-4-5 specifies 42 Ω as the generator impedance.

The extremely high suitability of SIOV varistors for ensuring immunity to interference can be seen in table 2a:

Even for test severity level 4 (4 kV via 2 Ω), the very cost-efficient model S20 (type S20K275) is adequate. Here the "overvoltage" of 4 kV is reduced to a maximum of 900 V.

**Table 2a**

		<b>230 V rms</b>					
		Connection via					
		2 Ω			12 Ω		
		10 load cycles			10 load cycles		
Severity level	kV	Type	$i_{\max}$ A	$v_{\max}$ V	Type	$i_{\max}$ A	$v_{\max}$ V
1	0,5	Overvoltage protection not required					
2	1	S07K275	135	820	S05K275	28	790
3	2	S10K275	590	920	S07K275	110	830
4	4	S20K275	1560	900	S07K275	270	850

**Table 2b**

		<b>400 V rms</b>					
		Connection via					
		2 Ω			12 Ω		
		10 load cycles			10 load cycles		
Severity level	kV	Type	$i_{\max}$ A	$v_{\max}$ V	Type	$i_{\max}$ A	$v_{\max}$ V
1	0,5	Test makes no sense					
2	1	S05K460	3	1000	S05K460	2	990
3	2	S10K460	360	1430	S05K460	60	1450
4	4	S20K460	1300	1530	S07K460	230	1410

## Application and Design Examples

---

### Selection example

How to determine suitable varistors for each case covered by tables 2a and b is demonstrated by the example of the S20K275.

#### Operating voltage

According to IEC 38, from the year 2003 onwards the operating voltage tolerance in Europe will be 230 V ± 10%, i.e. a maximum operating voltage of 253 V can be expected. This means that only varistors of the voltage classes “K275” (or higher) may be selected.

#### Surge current

The surge current caused by the hybrid generator depends to a large extent on the load, i.e. on the varistor, in this case. It is easy to determine amplitude and current duration by simulation. Here, one should take into account that the greatest current flows across the varistor whose *V/I* characteristic is at the lower limit of the tolerance band.

In this case, the resulting current amplitude for S20K275 is approx.  $\hat{i}^* = 1560$  A, the current duration of the equivalent rectangular wave is < 20 μs. For 10 repetitions, the value of ( $t_r \leq 20$  μs)  $i_{\max} = 2500$  A can be deduced from the derating curve for S20K275.

Since  $i_{\max} > \hat{i}^*$  the selection criterion for the surge current is fulfilled.

If no simulation is available, then the surge current has to be determined by a test circuit or by mathematical approximation.

The approximation solution (equation 12) results in:

$$\hat{i}^* = \frac{V_s - V_{\text{SIOV}}}{Z_{\text{source}}} = \frac{4000 - 750}{2} = 1625 \text{ A} < i_{\max}$$

A maximum value of 940 V is obtained from the *V/I* characteristic for the S20K275 at 2000 A; the lower tolerance limit will then be approx. 940 V – 20 %.

The current duration can be estimated on the basis of the fact that the hybrid generator produces a short-circuit surge current wave of 8/20 μs. Under load with a low-resistance varistor one can expect a waveform similar to that of the 8/20 μs wave, whose transformation into an equivalent rectangular wave has a  $t_r^* < 20$  μs. Again this leads to a reading of  $i_{\max} = 2500$  A for 10 times in the derating curve. With  $\hat{i}^* = 1625$  A <  $i_{\max}$  the selection criterion of equ. 9 is fulfilled. The difference between the results of this calculation and the simulation results is negligible.

#### Energy absorption

The energy absorption of the S20K275 varistor can be calculated directly by simulation.

It is possible to estimate the value by means of equation 15 (lower tolerance field limit):

$$W^* = \hat{v}^* \hat{i}^* t_r^* = 750 \cdot 1625 \cdot 20 \cdot 10^{-6} = 24 \text{ J}$$

## *Minimum time interval between energy loads*

The minimum time interval between loads to the S20K275 can be deduced from equation 19:

$$T_{\min} = \frac{W^*}{P_{\max}} = \frac{24 \text{ J}}{1 \text{ W}} = 24 \text{ s}$$

## *Protection level*

The highest possible protection level, which the S20K275 will achieve, can be deduced from the + 10 % tolerance curve simulation. According to table 2a, the maximum voltage  $v_{\max}$  is 900 V.

Similar results are obtained for a current of approx. 1600 A in the V/I characteristic curve field.

### **3.2.5 Interference emission**

The switching off inductive loads can lead to overvoltages which may become sources of line interference as well as of inductively and/or capacitively coupled interference. This kind of interference can be suppressed using varistors connected as a fly-wheel circuit.

SHCV varistors are especially well-suited for radio-frequency interference suppression.

### **3.2.6 EMC systems engineering**

S+M Components is your competent partner when it comes to solving EMC problems.

Our performance range covers

- systems for measuring and testing EMC
- shielded rooms for EMP measures
- anechoic chambers
- EMC consultation services and planning

For further details, please refer to the EMC Components Data Book (ordering no. B424-P2414-X-X-7600).

## **3.3 Protection of automotive electrical systems**

### **3.3.1 Requirements**

Electronic equipment must work reliably in its electromagnetic environment without, in turn, unduly influencing this environment. This requirement, known as electromagnetic compatibility (EMC), is especially important in automotive electrical systems, where energy of mJ levels is sufficient to disturb or destroy devices that are essential for safety. S+M Components has devised a wide range of special models matched to the particular demands encountered in automotive power supplies:

- extra high energy absorption (load dump)
- effective limiting of transients
- low leakage current
- jump-start capability (no varistor damage at double the car battery voltage)
- insensitive to reverse polarity
- wide range of operating temperature
- high resistance to cyclic temperature stress
- high capacitance for RFI suppression




## 3.3.4 Tests


Maintenance of EMC requirements can be checked with conventional test generators. Figures 29a and b show block diagrams for load dump tests with operating voltage applied. The electrical performance associated with a load dump of 100 J is illustrated in figures 30a to c.

### Note

Circuit 29b produces the test pulse according to ISO 7637-1 (DIN 40 839); the 10 % time constant  $t_{d10}$  can be set independently of the battery voltage. Note that the maximum discharge current is not limited by the source  $V_{DC}$ .

 


**Figure 29a** Principle of load dump generator with battery connected in parallel

 

**Figure 29b** Principle of load dump generator with battery connected in series

# Application and Design Examples


30a

 

Test pulse 5  
acc. ISO 7637-1  
(DIN 40 839)

VAR0143-L

30b

 


Example:

$C_0$	37,6 mF
$R_0$	4,6 $\Omega$
$C_1$	47 $\mu$ F
$V_S$	146 V
$V_{DC}$	14 V
$R_i$	2 $\Omega$
$t_d$	400 ms
$t_r$	0,1 ms

VAR0144-U

30c

 


VAR0145-3

**Figure 30a – c** Voltage (b), current and energy absorption (c) on SIOV-S20K14AUTO with test pulse 5 (a), load dump generator as in figure 29 b

## 3.3.5 RFI suppression

The capacitance of varistors alone (some nF) is not enough for RFI suppression. Therefore S+M has developed the high-capacitive varistors SHCV (Siemens Matsushita HiCap Varistors) that offer transient protection and RFI suppression in very compact form. These components are comprised of a multilayer varistor connected in parallel with a multilayer capacitor. SHCVs are especially suitable for handling RFI from small motors of windscreen wipers, power windows, memory seats, central locking, etc. Figure 31 shows an example of the suppression effect.

 

**Figure 31** Example of RFI suppression in small motors with chokes and SHCVs (measured to VDE 0879, part 3)

## 3.4 Telecom

### 3.4.1 Requirements

Electromagnetic interference on telecommunications, signal and control lines can be quite considerable as these lines tend to be long and exposed. So the requirements are correspondingly high when it comes to the electromagnetic compatibility of connected components or equipment.


According to the directives of the Deutsche Telekom, the interference or noise immunity of equipment is tested by application of a surge voltage with a wave form according to CCITT and IEC 1000-4-5. Figure 32 shows a simplified circuit diagram. The test is made with five pulses of either polarity, at least 60 s apart. According to equation 12, a voltage of 2 kV produces a surge current amplitude of approx. 45 A. SIOV varistors are capable of handling this surge current (and of absorbing the accompanying energy).

## Application and Design Examples

The choice of voltage class will depend on

- minimum required resistance in undisturbed operation
- maximum permissible protection level at 45 A.

 Both figures can be derived from the  $V/I$  characteristics. (example of application 3.5.2).



e. g. telephone terminal device  
DUT Device under test

**Figure 32** Circuit for generating 10/700  $\mu$ s test pulse to CCITT and IEC 1000-4-5

### 3.4.2 Telecom varistors

If requirements for minimum resistance and protection level cannot be met by standard types, it is possible to specify an application-oriented type. In such cases the tolerance bandwidth at 1 mA is of no interest, so it is not stated for telecom varistors.

The following special types have gone into wide use:

Design	Type	Ordering code	$R_{\min}$ (95 V)	$v_{\max}$ (45 A)
Disk	SIOV-S07S60AGS2	Q69X3815	250 k $\Omega$	200 V
SMD	SIOV-CU4032S60AG2	Q69660-M600-S172	250 k $\Omega$	200 V
SMD	SIOV-CN1812S60AG	Q69580-V600-S162	250 k $\Omega$	200 V

Design	Type	Ordering code	$R_{\min}$ (150 V)	$v_{\max}$ (45 A)
Disk	SIOV-S07S95AGS2	Q69X4574	150 k $\Omega$	270 V
SMD	SIOV-CU4032S95AG2	Q69660-M950-S172	150 k $\Omega$	270 V
SMD	SIOV-CN1812S95AG2	Q69580-V950-S172	150 k $\Omega$	270 V

Contact us if these types do not meet your requirements; we offer design to customer specifications.


## 3.5 S+M's PSpice simulation model

### 3.5.1 Varistor model

The development of an SIOV model for the “PSpice Design Center” circuit simulation program allows varistors to be integrated into the computer-assisted development of modern electronic circuitry.

In the PSpice modelling concept, the varistor is represented by its  $V/I$  characteristic curve, a parallel capacitance and a series inductance.

The structure of this equivalent circuit is shown in figure 33.

 

**Figure 33** Varistor model, basic structure

In the model, the  $V/I$  characteristic curve is implemented by a controlled voltage source  $V = f(I)$ . An additional series resistance  $R_S = 100 \mu\Omega$  has been inserted in order to prevent the unpermissible state which would occur if ideal sources were to be connected in parallel or the varistor model were to be connected directly to a source.


The following approximation is used for the mathematical description:

$$\log V = b1 + b2 \cdot \log(I) + b3 \cdot e^{-\log(I)} + b4 \cdot e^{\log(I)} \quad I > 0 \quad (\text{equ. 20})$$

This means that the characteristic curve for any specific varistor can be described by the parameters  $b1 \dots b4$ . Figure 34 shows the typical  $V/I$  characteristic curve for the varistor SIOV-S20K275 and the corresponding parameters  $b1 \dots b4$ .

The tolerance bandwidth of the  $V/I$  characteristic curve can be shifted (cf. [figure 7](#)) in order to include cases of

- upper tolerance bandwidth limit:  
highest possible protection level for a given surge current, and
- lower tolerance bandwidth limit:  
highest possible (leakage) current for a given voltage.

 

**Figure 34** V/I characteristic curve of SIOV-S20K275 with tolerance band

In the model, the capacitance values stated in the product tables are used. The dependence of the capacitance on the applied voltage and frequency is extremely low and can be neglected here.

It is not permissible to neglect the inductance of the varistor in applications with steep pulse leading edges. For this reason, it is represented by a series inductance and essentially is determined by the lead inductance. As opposed to this, the internal inductance of the metal oxide varistor may be neglected. The inductance values in the model library are chosen for typical applications, e.g. approx. 13 nH for the S20K275. If longer leads are used, insertion of additional inductances must be considered, if necessary. In the case of disk varistors, the inductance of the leads is approx. 1 nH/mm.

The PSpice simulation models (Version 6.1 for Windows 3.2) can be obtained from S+M together with a data book. Ordering code: B462-P6214-V1-X-7600.

They can also be downloaded from the INTERNET (WWW) under <http://www.siemens.de/pr/index.htm>.

*Limits of the varistor model*

For mathematical reasons, the V/I characteristic curves are extended in both directions beyond the current range (10  $\mu$ A up to  $I_{max}$ ) specified in this data book, and cannot be limited by the program procedure. The validity of the model breaks down if the specified current range is exceeded. For this reason, it is imperative that the user takes consideration of these limits when specifying the task; the upper limit depends on the type of varistor. Values of < 10  $\mu$ A may lead to incorrect results, but do not endanger the component. In varistor applications, it is only necessary to know the exact values for the leakage current in the < 10  $\mu$ A range in exceptional cases. As opposed to this, values exceeding the type-specific surge current  $I_{max}$ , may lead not only to incorrect results in actual practice but also to destruction of the component. Apart from this, the varistor model does not check adherence to other limit values such as maximum continuous power dissipation or surge current

deratings. In addition to carrying out simulation procedures, the adherence to such limits must always be ensured, observing the relevant spec given in the data book.

In critical applications, the simulation result should be verified by a test circuit.


The model does not take into account the low temperature coefficient of the varistors (equ. 7).

### 3.5.2 Application example

In accordance with CCITT /IEC 1000-4-5, the test pulse 10/700  $\mu$ s is frequently used to ensure the interference immunity of equipment used in telecommunications applications. Five load pulses of each polarity are required, with a minimum interval of 60 s between loads. This test pulse is defined by the circuit of the test generator and the open-circuit voltage. Figure 32 shows the circuit of the test generator, figure 35 the implementation in PSpice.

In order to achieve an open-circuit voltage of 2 kV, the charging capacitor must be charged to 2,05 kV. In order to prevent an undefined floating of  $R_{m2}$ , an additional resistor  $R_1 = 10$  M $\Omega$  is inserted at the output end.

The voltage level "K95" is given as an example. The suitability of S10K95 for the test pulses is to be tested.

 

**Figure 35** Simulation of the test pulse 10/700  $\mu$ s applied to the device under test S10K95

For the varistor, the upper characteristic curve tolerance (TOL = +10) limit is used to simulate the worst case i.e. highest possible protection level. It is not considered necessary to model the device to be protected in this diagram, since, in relation to the varistor, this is generally of higher resistance for pulse loads.

Figure 36 shows the curve of the open-circuit voltage (varistor disconnected) and the maximum protection level (with varistor).

#### Surge current

Figure 37 shows the voltage and current curves, with the  $\int i^* dt$  included in the drawing.

A maximum current of 44 A can be deduced from the curves.

## Application and Design Examples

Then, according to equation 14:

$$t_r^* = \frac{\int i^* dt}{\hat{i}^*} = \frac{17 \text{ mAs}}{44 \text{ A}} \approx 386 \mu\text{s}$$

According to figure 38, the resulting maximum surge current for 10 loads is  $i_{\max} = 48 \text{ A} > \hat{i}^* = 44 \text{ A}$ .  
The selection criterion of equ. 9 is fulfilled.

### Energy absorption

PSpice displays the energy absorption directly as  $W^* = \int v^* i^* dt = 4,2 \text{ J}$ .

The resulting permissible time interval between two pulses according to equ. 19 is:


$$T_{\min} = \frac{W^*}{P_{\max}} = \frac{4,2 \text{ J}}{0,4 \text{ W}} = 10,5 \text{ s}$$

This means that the requirement of a minimum time interval between pulses of 60 s or more is fulfilled.

### Highest possible protection level

Figure 36 shows the highest possible protection level to be 260 V. Thus it is possible to reduce the "overvoltage" of 2 kV to 13 % of its value.

**Note:** The specification stated above can also be met using the specially developed telecom varistors (cf. section 3.4.2).

 

**Figure 36** Open-circuit voltage (varistor disconnected) and maximum protection level (with varistor) achieved by the SIOV-S10K95 varistor

 


Figure 37 PSpice simulation: voltage, current and  $\int i^* dt$  curves for the S10K95

 


Figure 38 A maximum surge current  $i_{max} = 48$  A (10 times) can be deduced for  $t_r^* = 386$   $\mu s$  from the derating curves for S10K50 ... 320

### 3.6 High-performance varistors for power electronics

The introduction of the first semiconductor components more than 30 years ago ushered in an era of rapid electronics development. With the emergence of high-performance thyristors, in particular of GTO (Gate Turn Off) thyristors in the mid-eighties, power electronics technology began to establish itself in fields from which it had been excluded up to then: since then, applications in high-performance power converters and pulse-width-modulated inverters for railway vehicles are state-of-the-art.

With the wide distribution of high-performance semiconductors and the compressing of ever higher power ratings into ever smaller volumes, overvoltage protection has also attained a significant role. Admittedly, the risk of damage can be limited by appropriate dimensioning of the individual components. However, in most cases this approach fails due to the over-proportionately increased costs for semiconductor components with higher power ratings. A ratio of  $\leq 2,5$  has proved to be satisfactory as a safety factor between the maximum overvoltage to be expected and the highest periodic peak inverse voltage ( $V_{DSM}$  or  $V_{RRM}$ ) in many applications. If there is a risk of overvoltages exceeding the level given by the selected safety factor, the use of an overvoltage protection circuit is necessary.

In the field of power electronics, the types of overvoltages can be categorized into the following groups:-

- overvoltages due to carrier storage effect (CSE)
- overvoltages caused by surge voltage waves
- switching transients

RC-elements, protective thyristors and protective diodes as well as voltage-dependent resistors have become the most commonly used protective elements.

#### *Overvoltage protection with varistors*

In the early days of power electronics, applications were frequently equipped with selenium overvoltage limiters. These components were available in various plate sizes and the size of the plate was determined by the maximum permissible peak current.

With the introduction of block varistors, components which showed considerably better performance with respect to leakage current and protection level became available.

In some application cases, block varistors in conventional housings still had the disadvantage that their continuous power dissipation capability was lower than that of selenium limiters.

#### *PowerDisk*


In order to increase the capability of handling periodic continuous loads, S+M Components has developed the PowerDisk, incorporating SIOV technology into a disk diode housing. The advantages of the construction translate into:

- excellent thermal conductivity
- easy mounting
- mechanical reliability
- high immunity to environmental influences

This means that the same mounting and cooling methods can be used for PowerDisks as for power semiconductors.

The PowerDisk PD80, when cooled on both faces, can dissipate 100 W, fifty times as much as the corresponding block varistor series B80. Upon special request, the PowerDisks can be supplied with the same operating voltages as the type series SIOV-B80. In this data book only the SIOV-PD80K1100 is specified.

Figure 39 shows the typical voltage and current as a function of time for a PowerDisk with 100 W power dissipation.

 

**Figure 39** PowerDisk with power dissipation of approx. 100 W

# Application and Design Examples

---

## 3.7 Combined circuits

### 3.7.1 Stepped protection

If transient problems cannot be resolved with a single component like a varistor, it is always possible to combine different components and utilize their respective advantages. As an example, figure 40 illustrates the principle of stepped protection of a telemetering line with a gas-filled surge arrester [1], a varistor and a suppressor diode\*):

The voltage of 10 kV is limited in three stages

- "coarse" surge arrester
- "standard" varistor
- "fine" suppressor diode, zener diode or filter [2]

to less than 50 V. The series inductors or resistors are necessary to decouple the voltage stages. For more details refer to Siemens publication [3].

#### *Note*

According to the specifications in [1] gas-filled surge arresters may not be used on low-impedance supply lines.

A PROTECTOR TESTER is available to test the function state of the above-mentioned protection components. This can be ordered using ordering code B84298-P1-A1.

### 3.7.2 Protective modules

Application-specific circuits for stepped protection assembled as modules, some incorporating overload protection and remote signaling, are available on the market.

Figures 41 a and b show some practical examples.


---

[1] Shortform catalog "Gas-Filled Surge Arresters", ordering no. B448-P4806-X-X-7400

[2] Data book "EMC Components", ordering no. B424-P2414-X-X-7600


[3] Pigler, Franz "EMV und Blitzschutz leittechnischer Anlagen" (only available in German), ordering no. A19100-L531-F503, ISBN 3-8009-1565-0

\*) Not in the S+M range

 


**Figure 40** Principle of stepped protection with surge arrester, varistor and suppressor diode

  **41a**



**41b**



**Figures 41a and b** Examples of transient protective modules

- Circuit with coarse protection plus fine transverse voltage protection
- Circuit with coarse protection plus fine longitudinal voltage and transverse voltage protection



Siemens Matsushita Components

European technology center for  
ceramic components

# There when you need us

This is an organization that's proven its worth. Because it stands for more customer proximity and thus better service. Here you get information straight from the source, implementation of the latest technologies and products that match the market. Concentration of resources means that design engineers and production engineers are working side by side. And SCS warehousing directly at the plant ensures fastest possible delivery.



**SCS – dependable, fast and competent**

