

2. Crosstalk reduction and shielding techniques

Crosstalk reduction

- Technology
- Layout, driver sizing
- Tolerant circuits



Shielding

3. References

Crosstalk reduction: technology

There are four sides to consider to reduce the effects of crosstalk:

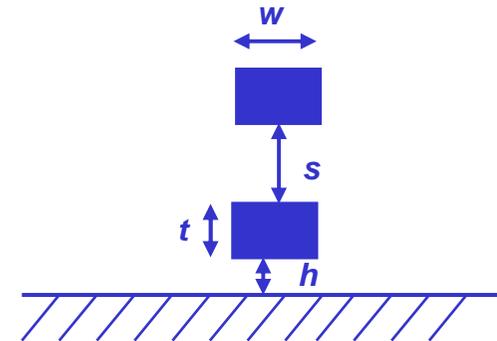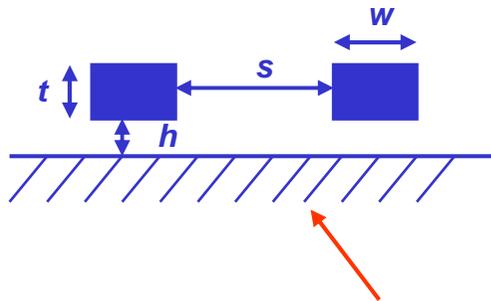- Technology
- Layout, driver sizing
- Design tolerance



Approximation


$$\begin{aligned}
 C_L &\approx \epsilon_{OX} \frac{lw}{h} \\
 C_C &\approx \epsilon_{OX} \frac{lt}{s}
 \end{aligned}
 \Rightarrow
 \Delta V \approx \frac{V_{DD}}{1 + \frac{C_L}{C_C}}
 \quad
 \frac{C_L}{C_C} \approx \frac{ws}{ht}$$

- $w \uparrow$ → delay
- $h \downarrow$ → delay
- $s \uparrow$ → area
- $t \downarrow$ → technology

Crosstalk reduction: layout

Scenarios (ITRS05)

	2007	2010	2013	
Local wiring pitch	156	90	64	[nm]
Intermediate wiring pitch	167	90	64	
Global wiring pitch	250	135	96	
Local wiring aspect ratio	1.7	1.8	1.9	t/w
Intermediate wiring aspect ratio	1.6	1.7	1.8	
Global wiring aspect ratio	2.1	2.3	2.4	

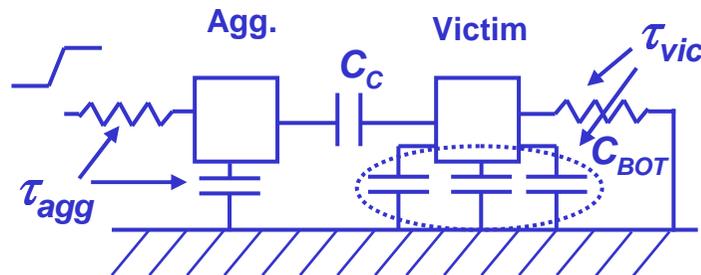

Simple model. Not capture distributed effects.
Wire resistance lumped with driver resistance.

(Ho01)

$$\Delta V = \frac{V_{DD}}{1 + \frac{C_{BOT}}{C_C}} \cdot \frac{1}{1 + \frac{\tau_{agg}}{\tau_{vic}}}$$


Ratio of driver strengths

- Line width → increases C_{BOT}
- Distance and screening → decreases C_C
- Driver strength → $\frac{\tau_{agg}}{\tau_{vic}} = 2$ to 4

Small influence for long interconnects


Crosstalk tolerant design: example

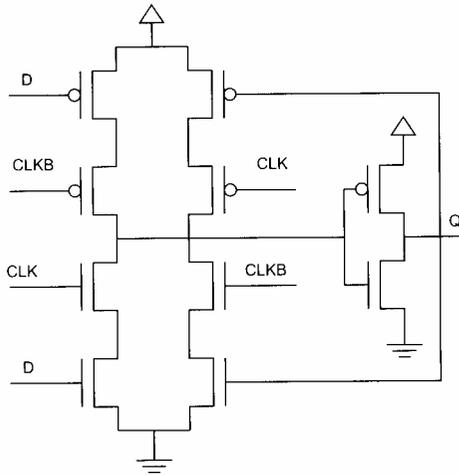CLK = 0 transparent state, CLK = 1 latch state
 CLKB = nCLK



Conventional latch

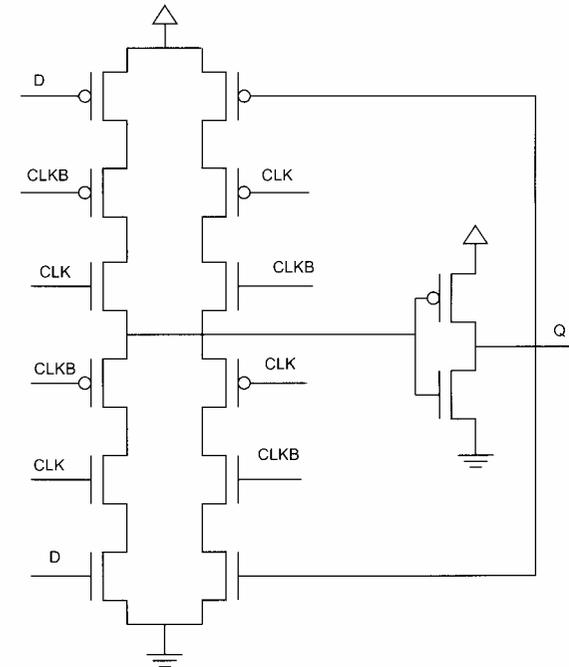CLK = 0 (CLKB=1) and D goes to 0 while the latch stores a 1. CLK and CLKB have a positive glitch, the latch can store a wrong "0"




Crosstalk tolerant latch [Rubio92]

Crosstalk reduction: length and number of aggressors


Crosstalk increases with number of aggressors, but tends to saturate with length

Arbitrary units

Crosstalk reduction: repeater insertion

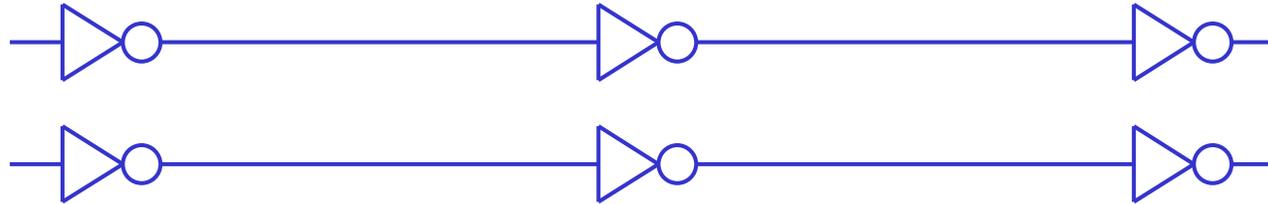

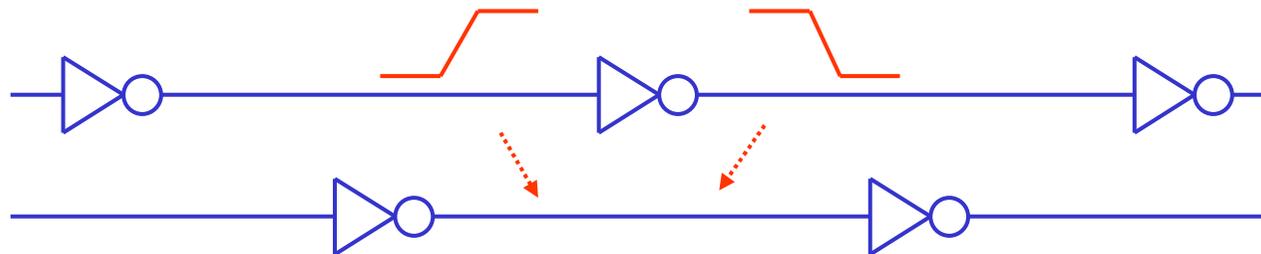Insertion of repeaters decrease crosstalk




Interleaved repeaters gives a further reduction

Optimization for delay and consumption

Shielding: crosstalk peak noise

Arbitrary units

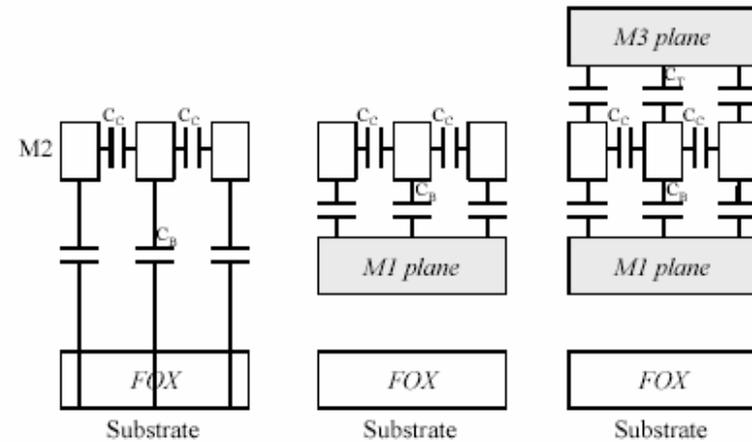

Planes are ideal conductors at zero potential

2, 4 or 6 aggressors equally distributed at both sides of the victim line

Worst case: same transition in all aggressors

Shielding: propagation delay

Worst case delay: opposite transitions in victim and aggressors (2)

Typical case delay: only transition in victim line

Best case delay: same transition in all lines

Shielding: delay noise

Delay noise = worst case delay – best case delay

Shielding: conclusions

Highest robustness: bus with top and bottom planes and wider spacing (at cost of lower performance)

Several basic references on crosstalk

- F. Moll, M. Roca, *Interconnection Noise in VLSI Circuits*, Kluwer 2004
- C.R. Paul, *Analysis of Multiconductor Transmission Lines*, Wiley 1994
- T. Sakurai, “Closed-Form Expressions for Interconnect Delay, Coupling and Crosstalk in VLSI’s”, *IEEE Transactions on Electron Devices*, Vol 40, No 1, January 1993, pp. 118-124
- J.A. Davis, J.D. Meindl, “Compact Distributed RLC Interconnect Models – Part I: Single Line Transient, Time Delay, and Overshoot Expressions”, *IEEE Transactions on Electron Devices*, Vol 47, No 11, November 2000, pp. 2068-2077.
- J.A. Davis, J.D. Meindl, “Compact Distributed RLC Interconnect Models – Part II: Coupled Line Transient Expressions and Peak Crosstalk in Multilevel Networks”, *IEEE Transactions on Electron Devices*, Vol 47, No 11, November 2000, pp. 2078-2087.
- A. Deutsch, G. V. Kopcsay *et al.*, “When are Transmission-Line Effects Important for On-Chip Interconnections?”, *IEEE Transactions on Microwave Theory and Techniques*, Vol 45, No 10, October 1997, pp. 1836-1846
- International Technology Roadmap for Semiconductors, Edition 2005, [http:// www.itrs.net](http://www.itrs.net)
- R. Ho, K.W. Mai, M. A. Horowitz, “The Future of Wires”, *Proceedings of the IEEE*, Vol 89, No 4, April 2001, pp. 490-504